

EXAMINATION QUESTIONS

(The authors are responsible for the answers)

CHAPTER I

(1) Show that the energy stored in a capacitor is given by the expression $\frac{1}{2}CV^2$.

An air capacitor of capacitance 0.005 microfarad is connected to a direct voltage of 500 volts, disconnected, and then immersed in oil with a dielectric constant of 2.5. Find the energy stored in the capacitor before and after immersion, and account for the difference. (Lond. Univ., Elec. Tech.)

Ans. Before immersion 625×10^{-6} J.; after immersion 250×10^{-6} J.

(2) A long straight cylindrical wire of very small diameter is suspended in free space and has on it a charge Q per unit length. Calculate directly from the inverse square law the strength of the electric field at a point far removed from the ends of the wire and at a distance x from the wire, where x is very large compared with the diameter of the wire. What will be the form of the equipotential surfaces and what will be the difference of potential between two points distant x_1 and x_2 from the wire?

If $Q = 0.00333$ microcoulomb per metre, $x_1 = 2$ cm and $x_2 = 20$ cm, what is the difference of potential in volts between the two points?

(Lond. Univ., Elec. Meas.)

Ans. 136 V.

(3) Calculate the strength of the magnetic field at the centre of a single-turn square coil of 1 ft side when carrying a current of 20 amp. Prove the formula employed.

Ans. 59 A/m.

(4) A solenoid is 2 ft long and 1 in. diameter, and is uniformly wound with 600 turns of insulated wire. Calculate the strength of the magnetic field at the centre when the current is 2 amp. If a secondary coil of 50 turns is wound round the central part of the solenoid and is connected to a ballistic galvanometer through a resistance which makes the total resistance of the circuit 10,000 ohms, calculate the quantity of electricity discharged through the galvanometer on reversing the current of 2 amp in the primary winding. Estimate the error due to assuming the solenoid infinitely long.

(Lond. Univ., Elec. Meas.)

Ans. 19.7×10^2 A/m; 1.25×10^{-8} coulomb; error 9 parts in 10,000.

(5) Draw diagrams showing the magnetic field around two parallel straight conductors carrying current (a) in the same direction, and (b) in opposite directions.

If two conductors 3 in. apart each carry 1,000 amp in the same direction, find the direction and magnitude per inch run of the force on each conductor.

(Lond. Univ., Elec. Tech.)

Ans. 6.78 grammes wt. (0.0666 newton) attraction.

(6) Two coils each of 20 cm diameter and 100 closely wound turns of fine wire are mounted coaxially 10 cm apart. A current of 1 amp is passed through the coils in series, the connections being such that the fields are additive. Plot a curve showing the field strength along the axis of the coils.

Prove any formula used.

(Lond. Univ., Elec. Meas.)

(7) The demagnetization curve for a sample of permanent-magnet steel after hardening and ageing is as follows—

Permanent flux density in webers per square metre	0.65	0.59	0.52	0.43	0.31	0.14
Demagnetizing ampere-turns per centimetre	4	12	20	28	36	44

The air-gap flux density in a moving-coil instrument where this steel is used is to be 0.09 Wb/m^2 , the length of the single gap is to be 0.12 cm , and the area of the gap 10 cm^2 . To ensure the necessary permanence, the ratio of the area of the gap divided by its length to the area of cross-section of the magnet divided by its length is to be 300. Assuming the leakage flux to be equal to the useful flux, and regarding all the leakage as being concentrated at the pole shoes, calculate the necessary length and cross-sectional area of the magnet.

To what extent is the above-mentioned ratio applicable to all permanent magnet steels?

Ans. 11.5 cm , 3.2 cm^2 .

(8) What are the criteria of the most suitable characteristics of a permanent magnet for use in a measuring instrument such as a moving-coil ammeter? Deduce the magnetic condition in which the permanent magnet should be operated in order that its volume may be a minimum, assuming given gap dimensions and flux density in the gap.

(*Lond. Univ., Elec. Meas.*)

CHAPTER II

(9) What is meant by the dimensions of a quantity? Derive the dimensions of potential difference in the electrostatic system in terms of Mass, Length, and Time.

In the course of a calculation an expression of the following form was arrived at—

$$I = E \left(\frac{1}{Z_1} + \frac{j\omega M}{Z_2} \left(\frac{1}{R} + \frac{C}{L} \right) \right)$$

Show that there must have been an algebraical error, and point out the term or terms which require correction.

(*Lond. Univ., Elec. Meas.*)

Ans. The term $\frac{C}{L}$ should be multiplied by some quantity having the dimensions of resistance (or impedance).

(10) The voltage V across the coils of a telephone receiver when a current I is flowing through them may be written

$$V = I \left(Z + \frac{A^2}{z} \right)$$

where $Z = R + j\omega L$

$$A = 2B_0 \frac{N}{\mathcal{R}}$$

$$z = r + j \left(\omega m + \frac{s}{\omega} \right)$$

R = the resistance

L = the inductance, and

N = the number of turns of the receiver coils

B_0 = the flux density in the air gap

\mathcal{R} = the reluctance of the magnetic circuit

and r , m , and s are the equivalent mechanical resistance, mass, and stiffness of the receiver diaphragm.

Suggest a suitable unit for each of the quantities involved.

Find the dimensions of each quantity, and so make a dimensional check of the equation. (Lond. Univ., Elec. Meas.)

Ans. Dimensions—

V — $[L^{\frac{1}{2}}M^{\frac{1}{2}}T^{-2}\mu^{\frac{1}{2}}]$	s — $[MT^{-2}]$
I — $[L^{\frac{1}{2}}M^{\frac{1}{2}}T^{-1}\mu^{-\frac{1}{2}}]$	A — $[L^{\frac{1}{2}}M^{\frac{1}{2}}T^{-1}\mu^{\frac{1}{2}}]$
Z — $[LT^{-1}\mu]$	B_0 — $[L^{-\frac{1}{2}}M^{\frac{1}{2}}T^{-1}\mu^{-\frac{1}{2}}]$
z — $[MT^{-1}]$	\mathcal{R} — $[L^{-1}\mu^{-1}]$
r — $[MT^{-1}]$	R — $[LT^{-1}\mu]$
m — $[M]$	L — $[L\mu]$

(11) (i) The expression for the mean torque T of an electrodynamic watt-meter may be written,

$$T \propto M^2 E^2 Z^t$$

where M = the mutual inductance between fixed and moving coils

E = applied voltage

Z = impedance of the load circuit.

From the dimensions of quantities involved determine p , q , and t .

(ii) In the same way, determine a , b , c , and g in the following expression for the eddy current loss W per centimetre length of round wire—

$$W \propto f^a B_{max}^b d^c \rho^g$$

where f = frequency

B_{max} = maximum flux density

d = diameter of the wire

ρ = resistivity of the material.

Ans. (i) $p = 1$, $q = 2$, $t = -2$; (ii) $a = 2$, $b = 2$, $c = 4$, $g = -1$.

(12) Give a concise account of the M.K.S. (Giorgi) system of units, and compare the advantages and disadvantages of this system with those of the C.G.S. electromagnetic system. (Lond. Univ., Elec. Meas.)

(13) What is meant by the "dimensions" of an electrical or magnetic quantity?

Obtain the dimensions of resistance and magnetic flux in the C.G.S. electro-magnetic system, and of charge and energy in the C.G.S. electrostatic system.

Briefly explain what is meant by a "rationalized" system of dimensions.

(Lond. Univ., Elec. Meas.)

CHAPTER III

(14) Three non-inductive resistances of 1,000 ohms are star-connected to a three-phase supply with 200 volts between lines. What will be the reading on a voltmeter connected between one of the lines and the star point thus formed, if the voltmeter also has a non-inductive resistance of 1,000 ohms? (Lond. Univ., Elec. Meas.)

Ans. 86.6 volts.

(15) An alternating current circuit contains a coil of inductance L_1 ; near this, but not connected to it, is a coil of inductance L_2 , across which is connected a resistance R . If the mutual inductance between the two coils is M , calculate the effective inductance and resistance of the first circuit.

(Lond. Univ., Elec. Meas.)

$$\text{Ans. Res.} = \frac{\omega^2 M^2 R}{R^2 + \omega^2 L_2^2}; \text{ ind.} = \left(L_1 - \frac{\omega^2 M^2 L_2}{R^2 + \omega^2 L_2^2} \right)$$

(16) An alternating current passes through a non-inductive resistance R and an inductance L in series. Find the value of the non-inductive resistance

which can be shunted across the inductance without altering the value of the main current.

(Lond. Univ., Elec. Meas.)

$$\text{Ans. } \frac{\omega^2 L^2}{2R}.$$

(17) The impedances of the three phases of a star-connected load (no neutral wire) are $5 + j20$, $12 + j0$, and $1 - j10$ in order. The line voltage is 400 volts. Find the line currents.

(Lond. Univ., Elec. Meas.)

$$\text{Ans. } 0.5 - 29.65j, 16.24 - 11.5j, -16.74 + 41.15j.$$

(18) Three branch circuits consisting respectively of (i) 5 ohms resistance and 0.025 henry inductance, (ii) 4 ohms resistance and 300 microfarads capacitance, (iii) 0.01 henry inductance and 500 microfarads capacitance, are connected in parallel. A resistance of 3 ohms is then connected in series with the combination. Using the symbolic "j" notation, calculate the currents in the main circuit, and in the three branches, when an alternating voltage $v = 100 \sin 314t$ is applied to the whole circuit.

$$\begin{aligned} \text{Ans. } i &= 20.2 \sin(314t + 37^\circ 55'), \\ i_1 &= 6.9 \sin(314t - 93^\circ 20'), \\ i_2 &= 5.64 \sin(314t + 33^\circ 35'), \\ i_3 &= 19.9 \sin(314t + 54^\circ 10'). \end{aligned}$$

(19) Two coils of self-inductance 0.01 henry and 10 henrys, and resistance 0.3 ohm and 300 ohms respectively, have a coefficient of coupling of 0.9.

Calculate the change in effective resistance of the first coil when a resistance of 100 ohms is connected to the terminals of the second, the frequency being 50 c/s.

(Lond. Univ., Elec. Meas.)

$$\text{Ans. } 0.318 \text{ ohm.}$$

(20) Explain the essential principle of the method of symmetrical components as applied to the solution of asymmetrical polyphase a.c. network problems.

Show how a direct measurement of the positive and negative sequence components of an unbalanced three-phase current system can be made. Give a diagram of connections and indicate what the observations signify with regard to the actual currents in the three lines.

(Lond. Univ., Elec. Meas.)

(21) Explain, with the aid of a diagram of connections, a method of measuring the symmetrical components of the currents in an unbalanced 3-phase, 3-wire system.

If in such a system the line currents, in amperes, are

$$I_r = 10 - j2; I_y = -2 - j4; I_b = -8 + j6$$

calculate their symmetrical components.

(Lond. Univ., Elec. Meas.)

$$\text{Ans. } I_{R0} = I_{Y0} = I_{B0} = 0.$$

$$I_{R1} = 7.89 + j0.732; I_{Y1} = a^2 I_{R1}; I_{B1} = a I_{R1}$$

$$I_{R2} = 2.113 - j2.732; I_{Y2} = a I_{R2}; I_{B2} = a^2 I_{R2}.$$

(22) An unbalanced star-connected load is supplied from symmetrical three-phase mains. The load impedances are Z_a , Z_b , Z_c and the positive phase sequence is a , b , c . Calculate the value of the positive phase-sequence current when the line voltage of the three-phase balanced supply is 400 V and $Z_a = 0 + j10 \Omega$, $Z_b = 0 - j5 \Omega$ and $Z_c = 10 + j0 \Omega$.

(Lond. Univ., Elec. Theory and Meas. Part III)

$$\text{Ans. } 36.6 \text{ A.}$$

CHAPTER IV

(23) Calculate the capacitance of a spherical capacitor if the diameter of the inner sphere is 20 cm, and that of the outer sphere is 30 cm, the space between

them being filled with a liquid with a relative permittivity of 2. Express your answer in microfarads.

Ans. $\frac{2}{3} \times 10^{-4}$ microfarad.

(24) A capacitor is made up of two parallel metal discs separated by three layers of dielectric of equal thickness but having relative permittivities of 2, 3, and 4 respectively. If the metal discs are 6 in. diameter and the distance between them 0.3 in., calculate the potential gradient in each dielectric and the total energy stored in each when a potential difference of 1,000 volts is applied between the discs.

Ans. 1,815, 1,210, 907.5 volts per cm; 13.51×10^{-6} , 8.98×10^{-6} , 6.755×10^{-6} J.

(25) Calculate the capacitance of the following system—

Two conductors $\frac{3}{8}$ in. diameter, and 400 yd long, lying parallel to each other and to an earthed plane, their height above the plane being 3 ft. The conductors are 3 ft apart.

Ans. 1,980 micromicrofarads.

(26) Capacitance measurements on a three-phase cable were made as follows—

Capacitance per mile between the sheath and one conductor connected together and the other two conductors connected together = 0.45 microfarad.

Capacitance per mile between the three conductors connected together and the sheath = 0.50 microfarad.

The potential between the conductors is 3,300 volts and the frequency is 50 cycles per second.

Find the charging current flowing to each conductor in a 20-mile length of the cable.

(*Lond. Univ., Elec. Meas.*)

Ans. 4.1 amp.

(27) Discuss the difficulties of constructing a standard capacitor for use in the high-voltage arm of a Schering bridge working on voltages above 100 kV.

A capacitor bushing forms arm *AB* of a Schering bridge, and a standard capacitor of 500 μF capacitance and negligible loss forms arm *AD*. Arm *BC* consists of a non-inductive resistance of 300 ohms. When the bridge is balanced, the resistance and capacitor in parallel in the remaining arm *CD* have values of 72.6 ohms and 0.148 μF respectively. The frequency is 50 c/s. Calculate from first principles the capacitance and the dielectric loss angle of the bushing.

(*Lond. Univ., Elec. Meas.*)

Ans. 121 μF ; $0^\circ 11.6'$.

CHAPTER V

(28) Annular shaped iron stampings are built up to form a ring 8 in. inside diameter and 10 in. outside diameter and 1 in. thick. The square cross-section is wound with 1,000 turns to form a toroidal coil. If the resistance of the wire is 200 ohms, and the relative permeability of the iron is 800, what current will flow under an impressed alternating voltage of 100 volts, 50 c/s?

What would be the effect of replacing the stampings by a solid iron core?

Ans. 0.288 amp.

(29) A ring 1 ft mean diameter is made of round iron 1 in. diameter, and is uniformly wound with 500 turns of copper wire 0.05 in. diameter. A second winding of 1,000 turns of wire 0.025 in. diameter is uniformly wound over the first. Assuming the iron to have a relative permeability of 800, calculate the

self-inductance of each winding and the mutual inductance between them; express your answers in practical units.

Ans. 0.133, 0.532, 0.266 henry.

(30) Define the practical unit of mutual inductance.

Two coils with terminals T_1T_2 and T_3T_4 respectively are placed side by side. Measured separately, the inductance of the first coil is 1,200 microhenrys, and that of the second coil is 800 microhenrys.

With T_2 joined to T_3 , the inductance between T_1 and T_4 is 2,500 microhenrys. What is the mutual inductance between the two coils, and what would be the inductance between T_1 and T_4 with T_2 joined to T_4 ?

Prove any formula used.

(*Lond. Univ., Elec. Tech.*)

Ans. $M = 250$ microhenrys, $L = 1,500$ microhenrys.

(31) A toroidal coil is uniformly wound with 250 turns. The core is of marble with a rectangular cross-section $2\frac{1}{2}$ in. deep and 2 in. wide; the outer diameter of the toroid is 6 in., and the inner diameter is 2 in.

Find the inductance of the toroid, proving any formula used.

(*Lond. Univ., Elec. Meas.*)

Ans. 0.873 millihenry.

(32) Explain the advantages of using a mutual inductance as a primary standard of inductance.

Estimate the mutual inductance between two parallel coaxial single-turn circular coils of diameter 40 cm and 4 cm respectively. The planes of the coils are 25 cm apart.


Justify the expressions used in this calculation.

(*Lond. Univ., Elec. Meas.*)

Ans. 0.00096 μ H.

CHAPTER VI

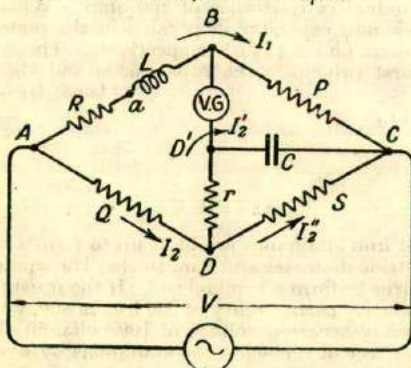(33) The diagram gives the connection of Anderson's bridge for measuring the inductance L and resistance R of an unknown impedance between the points A and B . Find R and L if balance is obtained when $Q = S = 1,000$ ohms, $P = 500$ ohms, $r = 200$ ohms, and $C = 2\mu$ F.



Draw a vector diagram showing the voltage and current at every point of the network when the voltage across AC is 10 volts and the frequency is 100 cycles per second.

(*Lond. Univ., Elec. Meas.*)

Ans. $R = 500$ ohms, $L = 1.4$ henrys.

(34) Explain how an inductance may be measured by comparison with a standard capacitor in an alternating-current bridge.

The four arms of a Wheatstone bridge arrangement are as follows: AB is an inductive resistance Lr_1 , BC is a non-inductive resistance r_2 , CD is a capacitor of capacitance C shunted by a resistance r_3 , DA is a non-inductive resistance r_4 . An alternating-current supply is connected between the points A and C and a telephone receiver across the points B and D . Work out the conditions for balance and show that the result is independent of the frequency of the supply.

(*C. and G. Final, Elec. Eng., II.*)

$$\text{Ans. } r_1 r_4 = r_2 r_3 = \frac{L}{C}$$

(35) In a balanced bridge network, AB is a resistance of 500 ohms in series with an inductance of 0.18 henry, BC and DA are non-inductive resistances of 1,000 ohms, and CD consists of a resistance R in series with a capacitance C . A potential difference of 5 volts at a frequency of $5,000/2\pi$ is established between the points A and C .

Draw to scale a vector diagram showing the currents and potential differences in the bridge, and from it determine the values of R and C .

Check the result algebraically.

(*Lond. Univ., Elec. Meas.*)

Ans. 472 ohms; 0.235 μF .

(36) It is required to measure the inductance and resistance of an iron-core choke of about 1 henry at frequencies varying from 50 to 3,000 c/s and with direct current flowing through it. An oscillator, standard capacitors, and non-inductive resistance boxes are available.

Describe a suitable a.c. bridge and detector, mentioning any precautions necessary to ensure accuracy in the result. Derive the equation of balance of the bridge used.

(*Lond. Univ., Elec. Meas.*)

(37) Describe a suitable a.c. bridge method for measuring, at a frequency of 500 cycles per second, the self-inductance and effective resistance of a coil of approximately 0.2 henry inductance and 5 ohms resistance. Draw the vector diagram for the balance conditions and give the equations for balance.

(*Univ. Lond., Elec. Meas.*)

(38) Describe briefly the construction and method of adjustment of one type of vibration galvanometer. Compare its advantages and disadvantages with those of a telephone receiver for use in a.c. measurements at various frequencies.

Derive an expression for the sensitivity of the tuned galvanometer, showing how it is dependent on frequency and damping.

(*Lond. Univ., Elec. Meas.*)

(39) A 4-arm unbalanced a.c. bridge is supplied from a source having negligible impedance. The bridge has non-reactive resistors of equal resistance R in adjacent arms. The third arm has an inductor of resistance R and reactance X , where X is numerically equal to R . The fourth arm has a variable non-reactive resistor. The detector is connected between the junction of the first and second arms and the junction of the third and fourth arms and has a resistance R and negligible reactance. Determine the value of the variable resistor when the detector current is in quadrature with the supply current.

(*Lond. Univ., Elec. Theory and Meas., Part III*)

Ans. $1.37 R$.

(40) A T-network has series arms AB and BD , each being a coil of inductance $3 \mu\text{H}$ and loss resistance 6Ω at 12 Mc/s. The shunt arm BE is a variable resistor R , and the series arms are bridged by a calibrated variable capacitor C connected between A and D . A voltage at 12 Mc/s is applied between A and E .

Show that there is one combination of R and C for which no voltage appears between D and E , and evaluate these two quantities.

An unknown capacitance connected between A and D can be measured by noting the change in C required to restore the null condition. Explain the advantages of this method. (Lond. Univ., Elec. Meas.)

Ans. $R = 4,250 \Omega$; $C = 29.4 \mu\mu\text{F}$.

(41) A balanced bridge has the following components connected between its five nodes, A, B, C, D and E —

Between A and B :	1,000 ohms resistance
" B " C :	1,000 " "
" C " D :	an inductor " "
" D " A :	218 ohms resistance
" A " E :	469 " "
" E " B :	10 μF capacitance
" E " C :	a detector
" B " D :	a power supply (a.c.)

Derive the equations of balance and hence deduce the resistance and inductance of the inductor. (Lond. Univ., Elec. Theory and Meas., Part III)

Ans. $R = 218 \Omega$; $L = 7.89 \text{ H}$.

CHAPTER VII

(42) The four arms of a Wheatstone bridge have the following resistances: AB 100, BC 10, CD 4, DA 50 ohms.

A galvanometer of 20 ohms resistance is connected across BD . Calculate the current through the galvanometer when a potential difference of 10 volts is maintained across AC . (Lond. Univ., Elec. Tech.)

Ans. 0.00513 amp.

(43) Describe the Kelvin double bridge for the comparison of small resistances.

Give the theory of the bridge, and detail the arrangements necessary in order that the greatest precision possible may be obtained.

(Lond. Univ., Elec. Meas.)

(44) Describe with a diagram of connections the loss-of-charge method of determining the insulation resistance of a length of cable. Prove the formula used for this determination, and calculate the insulation resistance of a short length of cable in which the voltage falls from 100 to 80 in 20 sec, the capacitance being 0.0003 microfarad. (Lond. Univ., Elec. Tech.)

Ans. 298,000 megohms.

(45) Describe a method by which the insulation resistance to earth of each of a pair of live mains can be measured by a voltmeter of known resistance. Discuss the limitations of the method.

The following readings were taken with a 250 volt, 1,000 ohms per [volt, voltmeter—

Between two mains	218 volts
Positive main to earth	188 volts
Negative main to earth	10 volts

Calculate the insulation resistance of each main.

(Lond. Univ., Elec. Meas.)

Ans. Positive 500,000 Ω ; negative 26,600 Ω .

(46) A moving-coil galvanometer has a sensitivity of 4 cm per micro-ampere, with a scale 1 metre distant, and the time of free oscillation is 2.8 sec.

If the galvanometer is dead beat when the total circuit resistance (coil and external circuit) is 2,500 ohms, find the moment of inertia of the moving system.

Prove any formula used.

(Lond. Univ., Elec. Meas.)

Ans. 2.7×10^{-7} kg-m².

(47) What is meant by critical damping, and to what extent should this condition be approached in the case of an ordinary moving-coil type of instrument?

The coil of a moving-coil galvanometer has 300 turns and is suspended in a uniform magnetic field of 0.1 Wb/m² by a phosphor-bronze strip, of which the torsion constant is 2×10^{-7} newton-metre per radian. The coil is 2 cm wide and 2½ cm high, with a moment of inertia of 1.5×10^{-7} kg-m².

If the galvanometer resistance is 200 ohms, calculate the value of the resistance which, when connected across the galvanometer terminals, will give critical damping. Assume the damping to be entirely electromagnetic.

Ans. 450 ohms.

CHAPTER VIII

(48) In the measurement of a low resistance by means of a potentiometer the following readings were obtained—

Voltage drop across low resistance under test	0.83942 volt
Voltage drop across a 0.1 ohm standard resistance connected in series with the "unknown"	1.01575 volt

The resistance of the standard at the temperature of the test is 0.10014 ohm. Upon setting the potentiometer dials to zero and breaking the current passing through the "unknown" resistance, the thermal e.m.f. of the latter produced a galvanometer deflection equivalent to 23 microvolts, the direction of the deflection being the same as that produced by an increase of the potentiometer reading during the voltage drop measurements.

Calculate the resistance of the "unknown."

Ans. 0.08276₆ ohm.

(49) Explain the principle of one type of co-ordinate a.c. potentiometer. Draw a diagram of the scheme of connections and describe how the potentiometer is standardized.

Measurements for the determination of the impedance of a coil were made on a co-ordinate potentiometer as follows—

Voltage across a 1 Ω standard resistance in series with the coil, + 0.952 V on in-phase dial, - 0.34 V on quadrature dial.

Voltage across a 10 : 1 potential divider connected to the terminals of the coil, + 1.35 V on in-phase dial, + 1.128 V on quadrature dial.

Calculate the resistance and the reactance of the coil.

Ans. $R = 8.82 \Omega$; $X = 15 \Omega$.

(Lond. Univ., Elec. Meas.)

(50) A current of 10 A at a frequency of 50 c/s was passed through the primary of a mutual inductor having a negligible phase defect. The voltages at the primary and secondary terminals were measured on a co-ordinate potentiometer and are given below.

With secondary winding open-circuited,	
secondary volts	- 2.72 + j 1.57
primary volts	- 0.211 + j 0.352

With secondary winding short-circuited,	
primary volts	- 0.051 + j 0.329

The phase of the primary current relative to the potentiometer current was the same in both tests.

Determine the self- and mutual inductances of the inductor.

(*Lond. Univ., Elec. Theory and Meas., Part III*)

Ans. $M = 1.0 \text{ mH}$, $L_1 = 0.114 \text{ mH}$, $L_2 = 18.06 \text{ mH}$.

(51) Describe two d.c.-a.c. transfer devices which might be used for standardizing a.c. potentiometers, one for low frequencies and the other for high frequencies. State the advantages and disadvantages of each device. Discuss the errors of potentiometer measurements at high frequencies.

(*Lond. Univ., Elec. Theory and Meas., Part III*)

CHAPTER IX

(52) What are the conditions to be fulfilled by a ballistic galvanometer? Describe the construction of such an instrument, and explain how to determine the constant and the logarithmic decrement.

The periodic time of an undamped reflecting ballistic galvanometer is 10 sec, and a current of 0.1 mA gives a steady deflection of 200 scale divisions. Find the quantity of electricity which produces a swing of 100 divisions. What is the quantity of electricity corresponding to this swing if the instrument has a decrement of 1.03?

(*C. and G. Final*)

Ans. 0.0000795 coulomb; 0.000121 coulomb.

(53) Explain carefully how the construction of a fluxmeter differs from that of a moving-coil ammeter or voltmeter.

A certain fluxmeter has the following constants—

Air-gap flux density, $5 \times 10^{-3} \text{ Wb/m}^2$.

Turns on moving coil, 40.

Area of moving coil, 7.5 cm^2 .

If a 10-turn search coil of 2 cm^2 area, which is connected to the fluxmeter, is reversed in a uniform field of flux density $5 \times 10^{-2} \text{ Wb/m}^2$, calculate the deflection of the meter.

Why is it necessary to keep the resistance of the moving coil, and of the search coil and leads, low? How may a correction for an unavoidably high resistance in the search coil be made?

Ans. $76\frac{1}{2}^\circ$.

(54) State the theory underlying the action of the Chattock magnetic potentiometer. Describe the instrument, and show how it can be calibrated and used in conjunction with a ballistic galvanometer for the measurement of difference of magnetic potential.

The constant of a given potentiometer was obtained by aid of a coil of 300 turns in which a current of 0.6 amp was reversed. The resulting throw of the galvanometer was 157 scale divisions. It was then used to measure the magnetic potential difference between two points and the throw was 304 scale divisions. Find the magnetic potential difference, and state the units in which it is measured.

(*Lond. Univ., Elec. Meas.*)

Ans. 695 amperes.

(55) Describe a method for finding the B - H curve of bar specimens.

An iron ring of 3.5 sq. cm cross-sectional area with a mean length of 100 cm is wound with a magnetizing winding of 100 turns. A secondary coil with 200 turns of wire is connected to a ballistic galvanometer having a constant of 1 microcoulomb per scale division, the total resistance of the secondary circuit being 2,000 ohms. On reversing a current of 10 amp in the magnetizing coil, the galvanometer gave a throw of 100 scale divisions. Calculate the flux density in the specimen and the value of the permeability at this flux density.

(*C. and G. Final*)

Ans. $B = 1.428$, $\mu_r = 1,136$.

(56) Describe a standard form of apparatus for measuring the iron losses in steel sheets at specified values of flux density and frequency by means of a wattmeter.

The following test results were obtained on a sample of steel stampings at 50 c/s—

Volts	Amperes	Watts
4.9	0.20	9.5
69.3	0.30	16.8
91.8	0.46	27.5
100.5	0.52	32.5
110.5	0.64	39.0
118.0	0.77	44.8

Mean width of the plates, 3 cm; mean thickness, 0.0489 cm; number of plates, 51; total weight, 24.2 lb; number of magnetizing turns in coil, 600. Allowing 2 watts copper loss in the magnetizing winding, calculate the iron loss in watts per pound at a flux density of 1 Wb/m², and 50 c/s.

Ans. 1.18 W/lb.

(57) Describe a method of using an a.c. potentiometer for measuring the loss in an iron ring made up of thin stampings. Explain how the loss may be calculated in terms of the maximum density, and state any assumptions made.

(*Lond. Univ., Elec. Meas.*)

CHAPTER X

(58) An open space is illuminated by four lamps each giving 300 candelas in every direction below the horizontal. They are suspended 23 ft above the ground at the corners of a rectangle 20 ft by 15 ft. Calculate the illumination in lumens per sq. ft of a horizontal surface 3 ft above the ground (a) at the middle of the shorter side, and (b) at the mid-point of the rectangle.

Describe briefly a portable photometer suitable for testing the accuracy of your calculations.

Ans. 1.72 lm/ft²; 1.83 lm/ft².

(59) Define the following terms: (a) mean spherical intensity; (b) lumen; (c) illumination; (d) brightness. What is the illumination at the edge of a circular table 6 ft in diameter lit by one 100 cd lamp 4 ft above the centre?

Ans. 3.2 lm/ft².

(60) Describe a good type of portable illumination photometer suitable for outdoor use; explain how it can be calibrated and discuss the various sources of error in its use.

If two lamps giving 500 candelas in every direction are suspended 30 ft high and 100 ft apart, compare the illumination of the horizontal road surface under one lamp with that midway between them.

Ans. 3.76 : 1.

(61) How would you determine the constants α and β in the expression

Luminous intensity = αV^β for a glow lamp, where V is the lamp voltage?

Taking the value $\beta = 4.5$ for a tungsten-filament vacuum lamp, determine the percentage variation of luminous intensity due to a voltage variation of ± 4 per cent from the normal value.

Ans. 19.2 per cent above normal, 16.75 below normal.

(62) A road is to be illuminated by means of lamps supported at a height of 20 ft, and arranged 100 ft apart. Determine the necessary distribution of luminous intensity in a vertical plane in order that the lamps may produce a uniform horizontal illumination on the ground along a line vertically beneath a pair of lamps. The illumination due to a lamp at a greater distance than 50 ft may be neglected.

Ans. $I_{\theta} = \frac{I_0}{\cos^3 \theta}$, where θ is the angle between the line vertically down through the lamp and the line joining the lamp to any point on the road between the lamps.

$I_0 = I$ vertically under a lamp.

(63) Define luminous flux, luminous intensity, and illumination, and state and define the units in which they are measured.

Describe the construction and use of a photo-electric photometer.

(64) Describe an apparatus by means of which the mean spherical intensity of a 1,000-watt gas-filled lamp can be determined by a single reading. Explain the principle involved and discuss the precautions which must be taken to ensure accuracy.

CHAPTER XI

(65) Describe with connection diagram how the peak value of a high voltage may be measured by means of a neon tube. Explain how the method is applied to the calibration of an extra-high-voltage voltmeter. How would you arrange to detect with certainty the striking of the neon tube?

(C. and G. Final)

(66) What methods may be used in testing cables for dielectric strength at very high voltages? Explain the difficulties that occur when tests with alternating voltages are made on long lengths of cable, and state what difference there is (if any) in the dielectric strength of (a) paper (b) air, when tested respectively with alternating and direct voltages.

(67) Describe an equipment for the production of high voltages for surge or impulse tests. Explain the action of the circuit described, and show precisely how the shape of the impulse wave can be controlled.

(C. and G. Final)

CHAPTER XII

(68) Describe the Murray loop method of localizing an earth fault on a length of cable.

In a test for a fault to earth on a 520 yd length of cable having a resistance of 1.10 ohms per 1,000 yd, the faulty cable is looped with a sound cable of the same length but having a resistance per 1,000 yd of 2.29 ohms. The resistances of the other two arms of the testing network, at balance, are in the ratio 2.7 : 1. Calculate the distance of the fault from the testing end of the cable.

Ans. 432 yd.

(69) Describe a method by which the position of a fault to earth on a long feeder may be found approximately by a "loop" test.

What methods may be used for finding the position of the fault when a break in the conductor occurs without affecting the insulation resistance very seriously?

CHAPTER XIII

(70) Show that, if α_1 be the resistance-temperature coefficient of a conductor at $t_1^\circ\text{C}$ expressed as a fraction, the coefficient at $t_2^\circ\text{C}$ is given by

$$\alpha_2 = \frac{1}{\frac{1}{\alpha_1} + (t_2 - t_1)}$$

A specimen of copper wire has a resistivity of 1.6×10^{-6} ohm-cm at 0°C , and a temperature coefficient of $\frac{1}{254.5}$ at 20°C . Find the temperature coefficient and the resistivity at 60°C .

(C. and G. Final)

Ans. $\frac{1}{294.5} \cdot 2.009 \times 10^{-6}$ ohm-cm.

(71) Describe a method for measuring the temperature rise in the field-magnet windings of a direct-current generator? Explain briefly how the final temperature rise of a machine may be estimated from the curve of temperature rise at the beginning of the heat run.

(72) Describe suitable methods for the measurement of the temperature of the following—

- The centre portion of the winding of a field coil on an electrical machine.
- A small quantity of molten metal.
- The interior of a furnace.

State why each method described is the most suitable for its purpose.

(73) Describe how the measurement of temperature can be made electrically—

- by thermocouples,
- by a bridge method suitable for moderately high temperatures,
- at very high temperatures.

Discuss the precautions necessary to avoid error in each case.

(Lond. Univ., Elec. Theory and Meas., Part III)

CHAPTER XIV

(74) An electromagnet of the type used for moving-coil loudspeakers has a central circular core and uniform air gap. The field in the air gap is uniform and radial. The electromagnet is arranged with the central core vertical so that an aluminium ring placed in the gap at the top of the central core could fall freely through the air gap under gravity. If the density of the radial flux is B and the ring has a cross-sectional area A with mean circumference L , and the material has a resistivity ρ and a density D , derive an expression for the velocity attained by the ring at any instant after it has begun to fall.

(Lond. Univ., Elec. Meas.)

Ans. $v = \frac{g\rho D}{B^2} \left[1 - e^{-\frac{B^2}{\rho D} t} \right]$.

CHAPTER XV

(75) An electromotive force, $e = 2,000 \sin \omega t + 400 \sin 3\omega t + 100 \sin 5\omega t$ is connected to a circuit consisting of a resistance of 10 ohms, a variable inductance, and a capacitance of 30 microfarads arranged in series with a

thermal ammeter. Find the value of the inductance which will give resonance with the triple-frequency component of the voltage and estimate the readings on the ammeter and on a thermal voltmeter connected across the supply when resonant conditions exist. ($\omega = 300$.)

Ans. 0.0411 henry; 31.7 amp; 1,442 volts.

(76) Derive an expression for the r.m.s. value of a complex wave-form of voltage.

Analysis of the wave-form of the voltage generated by an alternator shows that there are third and fifth harmonics having amplitudes equal, respectively, to 30 per cent and 20 per cent of that of the fundamental. The third harmonic lags behind the fundamental by 20 degrees and the fifth harmonic by 10 degrees. A dynamometer voltmeter connected to the alternator terminals gives the same reading as is produced by 150 volts d.c. Derive an expression for the instantaneous value of the voltage in the circuit.

(*Lond. Univ., Elec. Meas.*)

$$\text{Ans. } v = 200 \sin \omega t + 60 \sin \left(3 \omega t - \frac{\pi}{3} \right) + 40 \sin \left(5 \omega t - \frac{5}{18} \pi \right).$$

(77) Explain why alternating voltage and current wave-forms usually contain no even harmonics. In what practical instances may even harmonics occur?

A rectifier gives a current wave which has a sinusoidal form but with the negative half-wave completely suppressed. The maximum height of the wave is 100 amp. Determine (i) the steady component and (ii) the fundamental of the wave.

(*Lond. Univ., Elec. Meas.*)

Ans. 31.8 amp; $50 \sin \theta$.

(78) A voltage, represented by $300 \sin \omega t$ volts, is applied to a circuit consisting of a non-inductive resistance of 20 ohms in series with a luminous discharge lamp and produces a current represented by

$$(5 \sin \omega t - 2 \sin 3 \omega t) \text{ amp}$$

Calculate the power absorbed by the resistance and by the lamp; also the power factor of the lamp and of the complete circuit.

(*Lond. Univ., Elec. Meas.*)

Ans. 290 watts; 460 watts; 0.838; 0.93.

(79) Describe and give the theory underlying the operation of some form of electric harmonic analyser. A certain periodic wave that repeats itself every half-cycle is found to have ordinates y corresponding to angles θ degrees as follows—

θ	0	15	30	45	60	75	90	105	120	135	150	165	180
y	1.4	3.9	5.2	5.5	5.3	5.0	5.2	5.7	6.4	6.3	4.9	2.0	-2.7

Determine the amplitude and phase of the third harmonic present in the wave.

(*Lond. Univ., Elec. Meas.*)

Ans. 1.83, leading $22\frac{1}{2}^\circ$ relative to the fundamental.

(80) Explain how the amplitude of the harmonics in a supply voltage of complex wave-form may be determined experimentally with the aid of a dynamometer wattmeter and a beat-frequency oscillator of pure wave-form.

A single-phase load takes a current of

$$4 \sin \left(\omega t + \frac{\pi}{6} \right) + 1.5 \sin \left(3 \omega t + \frac{\pi}{3} \right) \text{ amperes}$$

from a source represented by $360 \sin \omega t$ volts. Calculate the power dissipated by the circuit and the circuit power factor. (*Lond. Univ., Elec. Meas.*)

Ans. 623.5 W; 0.837.

(81) A coil of 200 turns, wound on a rectangular former 10 cm long and 8 cm wide, is placed with its longer side parallel with and 5 cm distant from a current-carrying conductor, the plane of the coil being arranged so that it contains the conductor.

Calculate the e.m.f. induced in the coil by a current

$$i = 10 \sin 314t + 5 \sin 942t$$

flowing in the conductor. What is the mutual inductance between the coil and the conductor?

Ans. $e = -[0.012 \cos 314t + 0.018 \cos 942t]$; $M = 3.82$ microhenrys.

(82) A critically-damped Duddell oscillograph is required to reproduce the 13th harmonic of a 50 c/s wave with relative amplitude correct to within 2 per cent.

What should be the natural frequency of the movement?

What will the relative phase angle departure of the 13th harmonic be?

(*Lond. Univ., Elec. Meas.*)

Ans. 4,590 c/s; $16^\circ 7'$.

(83) Sketch and describe briefly the essential features of a cathode-ray tube and suggest a simple method of providing a time-base that is practically linear.

Derive an expression for the electrostatic deflection in centimetres per volt. State any approximations used. Assume that the screen is flat and perpendicular to the centre line of the tube and neglect fringing effects at the edges of the deflecting plates. (*Lond. Univ., Elec. Meas.*)

CHAPTER XVI

(84) A capacitor of capacitance C , charged to a voltage V , is discharged at $t = 0$ through a resistance R in series with a leaky capacitor of capacitance C_2 and leakage conductance G , initially uncharged. Derive an expression for the voltage that will develop across C_2 .

(*Lond. Univ., Elec. Theory and Meas., Part III*)

Ans. $v = \frac{V}{C_2 R (m_1 - m_2)} (e^{m_1 t} - e^{m_2 t})$

where m_1 and m_2 are the roots of the equation

$$D^2 + D \left[\frac{G}{C_2} + \frac{1}{C_2 R} + \frac{1}{CR} \right] + \frac{G}{RC_2 C} = 0$$

(85) Derive an expression for the current in a circuit containing resistance and inductance, due to an alternating voltage connected to the circuit at time $t = 0$.

If the resistance is 10.0 ohms, the inductance 2.5 henrys, and the circuit is connected to a 200 volt, 50 c/s supply at the instant when the voltage is a maximum, draw the first four cycles of the current wave.

(86) A sinusoidal voltage of 1,000 V and frequency 50 cycles per second is suddenly switched on to an inductive circuit of reactance 40 ohms and resistance 2.5 ohms. If the switch is closed when the instantaneous value of the voltage is zero, what will be the value of the current half a cycle later in time? (*Lond. Univ., Elec. Meas.*)

Ans. 4.01 A.

(87) Derive an expression from which the instantaneous current flowing in a circuit of inductance L and resistance R may be calculated at any time t after applying a voltage $V \cos(\omega t + \phi)$.

From the expression find the ratio of the maximum value to which the current rises to the steady-state maximum value, when the voltage is applied at the instant when it is zero, taking $R = 20$ ohms, $L = 0.1$ henry, and $\omega = 1,000\pi$.
(*Lond. Univ., Elec. Meas.*)

Ans. $i = \frac{V}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi + \alpha) + A e^{-\frac{Rt}{L}}$, where $\alpha = \tan^{-1} \frac{R}{\omega L}$
and A is a constant depending on the initial conditions; 1.8 (approx.).

(88) Two coils, A and B , have mutual inductance between them, coil A having an inductance of 1 H. When the two coils are connected in series, it is found that the total inductance is either 2.3 H or 0.7 H, depending upon the method of connection.

The series connection is now removed and a p.d. given by

$$v = 100 \sin 314 t \text{ volts}$$

is switched across A at an instant 10 milliseconds after the instant of zero voltage, B being on open circuit.

Assuming that the coils have no resistance, find (a) the maximum value of the current in A , (b) the value of the e.m.f. across B , 12 milliseconds after the switch was closed, and (c) the current in A at this instant.

Sketch the waveform of the primary current.

Deduce an expression (without evaluating it) for the current, if the coil A has resistance.
(*Lond. Univ., Elec. Theory and Meas., Part III*)

Ans. (a) 0.636 A; (b) 23.5 V; (c) 0.573 A.

CHAPTER XVIII

(89) The coil of a 150-volt moving-iron voltmeter has a resistance of 400 ohms and an inductance of 0.75 henry. The current drawn by the instrument when placed on a 150 volt d.c. supply is 0.05 amp. Estimate—

(a) The temperature coefficient of the instrument per degree centigrade.

(b) The alteration of the reading between direct current and alternating current at 100 c/s.

(c) The capacitance of the capacitor necessary to eliminate this frequency error. Show the method of connecting the capacitor.

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. 0.00066 ohm/ohm/°C; 1.17 per cent low at 100 c/s; 0.111 microfarad in parallel with the series resistance.

(90) Derive an expression for the torque of a moving-iron ammeter.

A resonating circuit was made by connecting a moving-iron ammeter in series with a $2.5 \mu\text{F}$ capacitor, and the resonance frequency, f in c/s, was determined with an ammeter deflection θ radians. It was found that f varied with θ in accordance with the expression

$$f = 1,000e^{-\theta/6}$$

The control torque of the ammeter is 11×10^{-6} newton-metre per radian. Determine the current in the circuit when $\theta = 1.5$ radians.

(*Lond. Univ., Elec. Theory and Meas., Part III*)

Ans. 77 mA.

(91) The control spring of a moving-iron ammeter exerts a torque of 5 dyne-cm per degree [5×10^{-7} newton-metre per degree], and the inductance of the coil varies with the pointer deflection according to—

Deflection (degrees)	20	40	60	80
Inductance (μH)	657	700	750	790

Determine the deflection produced by a current of 0.5 A.

Derive any expression used, and suggest a suitable method for measuring the variation of inductance with deflection.

(*Lond. Univ., Elec. Meas.*)

Ans. 31° .

(92) A moving-coil ammeter, a thermal ammeter, and a resistance of 100 ohms are connected in series with a rectifying device across a sinusoidal alternating supply at 200 volts. If the device has a resistance of 100 ohms to current in one direction, and of 500 ohms to current in the opposite direction, calculate the readings on the two ammeters, the power taken from the mains, and that dissipated in the rectifying device.

Ans. 0.3 amp; 0.74 amp; 133.3 watts; 77.8 watts.

(93) Give a sketch showing the construction of a moving-coil voltmeter.

If the moving coil consists of 100 turns wound on a square former which has a length of 3 cm and the flux density in the air gap is 0.06 Wb/m^2 , calculate the torque acting on the coil when it is carrying a current of 12 milliamp.

Ans. 0.66 g-cm (6.48×10^{-5} newton-metre).

(94) An instrument spring, constructed of phosphor-bronze strip, has the following dimensions: length of strip, 370 mm; thickness of strip, 0.073 mm; breadth of strip, 0.51 mm.

If E (Young's modulus for phosphor-bronze) be taken as $1.15 \times 10^6 \text{ kg per cm}^2$, estimate the approximate torque exerted by the spring when it is turned through an angle of 90° .

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. 0.0805 g-cm (0.79×10^{-5} newton-metre).

(95) The moving coil of a permanent-magnet ammeter is wound with 10 turns of copper wire, and has a resistance of 0.1 ohm. The total torque exerted by the control springs is 0.02 g-cm (1.96×10^{-6} newton-metre) per degree. When the terminals are connected to a Grassot fluxmeter, and a scale angle of 90° is traversed by the ammeter pointer, a linkage of 3×10^{-3} weber-turns is indicated.

Estimate the temperature coefficient of the ammeter when operating off a shunt having a drop of 0.075 volt at full load.

Ans. 0.00062 ohm/ohm/ $^\circ\text{C}$.

(96) State the causes of change of accuracy in moving-coil instruments with change of temperature. Explain how compensation is made in ammeters for change of electrical resistance of the moving coil with change of temperature.

It is required to construct a resistor of 5.0 ohms with a resistance-temperature coefficient of 8×10^{-5} per $^\circ\text{C}$. Platinoid and manganin wire of cross-sectional area 0.4 mm^2 are available and are to be connected in series. Calculate the lengths required if the resistivity of platinoid is 34.4 microhm-cm, and its resistance-temperature coefficient is 2.5×10^{-4} per $^\circ\text{C}$; corresponding figures for manganin are 48 microhm-cm, and 2×10^{-5} per $^\circ\text{C}$. All figures refer to 0°C .

(*Lond. Univ., Elec. Meas.*)

Ans. 151.3 cm platinoid.
308 cm manganin.

(97) A dynamometer ammeter is fitted with two field coils having a total resistance of 3.0 ohms and a total inductance of 0.12 henry, and a moving coil of resistance 30 ohms and inductance 0.003 henry. Calculate the temperature coefficient for changes of external temperature, and the error in reading when the instrument is calibrated with direct current and used on alternating current, 50 c/s, for each of the following arrangements—

(a) When the moving coil is shunted direct across the field coils.

(b) When the moving coil is shunted across a non-inductive resistance placed in series with the field coils.

(c) When connected as in (b), the non-inductive resistance having a value of 10 ohms, a suitable swamp resistance being placed in series with the moving coil.

(A.M.I.E.E., *Meters and Meas. Insts.*)

Ans. 0.004, 41.1 per cent low; 0.0024, 0.04 per cent low; 0.0006, 0.003 per cent low.

(98) Find the expression for the deflection of a quadrant electrometer in terms of the potentials of the two pairs of quadrants and the needle.

Hence explain the use of the instrument as (i) a voltmeter, and (ii) a wattmeter.

(99) Explain the action of a shaded-pole ammeter, showing by means of a sketch the direction of movement of the disc relative to the magnet poles. How is adequate damping secured, and how is the spread of the scale controlled? What are the advantages of this type of instrument for switch-board use, and to what errors is it subject?

(*Lond. Univ., Elec. Meas.*)

(100) Describe the principle and action of a shaded-pole motor. Explain how the torque is produced; show clearly in which direction it acts, and in what way it depends on the frequency.

How is the shaded-pole device applied in a.c. ammeters?

(*Lond. Univ., Elec. Meas.*)

(101) A metal rectifier is used for the measurement of a sinusoidal alternating current. The rectifier consists of four units arranged in bridge, each unit having approximate forward and reverse resistances of 5 ohms and 500 ohms respectively. The moving-coil indicator has a resistance of 20 ohms. Determine the indication when the r.m.s. input current is 4 milliamperes.

(*Lond. Univ., Elec. Meas.*)

Ans. 3.26 mA.

CHAPTER XIX

(102) A soft-iron voltmeter for a maximum reading of 120 volts has an inductance of 0.6 henry and a total resistance of 2,400 ohms. It is calibrated to read correctly on a 60 c/s circuit. What series resistance would be necessary to increase its range to 600 volts? Draw up suitable workshop instructions for making up the resistance.

(*Lond. Univ., Elec. Meas.*)

Ans. 9,660 ohms.

(103) The capacitance of an electrostatic voltmeter reading from 0 to 2,000 volts increases uniformly from 45 to 55 micromicrofarads as the pointer moves from zero to full-scale deflection. It is required to increase the range of the instrument to 20,000 volts by means of an external air capacitor.

Calculate the area of a pair of capacitor plates suitable for the purpose. If the capacitor is adjusted to make the full-scale reading correct, what will be the error per cent at half-scale reading?

(A.M.I.E.E., *Meters and Meas. Insts.*)

Ans. 175 sq. cm, assuming the distance between plates to be 2.5 cm; 8.9 per cent high.

(104) Discuss the reasons why the errors of a current transformer are usually greater with relatively small loads than at rated full load.

At its rated load of 25 VA, a 100/5-ampere current transformer has an iron loss of 0.2 W and a magnetizing current of 1.5 A. Calculate its ratio error and phase angle when supplying rated output to a meter having a ratio of resistance to reactance of 5.

(*Lond. Univ., Elec. Meas.*)

Ans. - 1.07 per cent; $0^\circ 45'$.

(105) Why is it important to use high-grade magnetic material for the laminations of current transformers? Discuss some of the advantages gained by substituting nickel-iron for silicon-iron in current transformer construction.

(*Lond. Univ., Elec. Meas.*)

(106) An 8/1 current transformer has an accurate current ratio when the secondary is short-circuited. The inductance of the secondary is 60 millihenrys and its resistance is 0.5 ohm, and the frequency is 50 c/s. Estimate the current ratio and phase-angle error when the instrument load has a resistance of 0.4 ohm and an inductance of 0.7 millihenry. State the assumptions made.

(*Lond. Univ., Elec. Meas.*)

Ans. 8.001; $0^\circ 2'$ assuming no iron loss, constant permeability, and magnetizing current = 1 per cent of primary current.

(107) A voltage transformer, ratio 1,000/100 volts, has the following constants—

Primary resistance	94.5 ohms
Secondary resistance	0.86 ohm
Primary reactance	66.2 ohms
Equivalent reactance	66.2 ohms
Magnetizing current	0.02 amp at 0.4 power factor

Calculate—

(i) The phase angle at no load between primary and secondary voltages.

(ii) The load in volt-amperes at unity power factor at which the phase angle will be zero.

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. $0^\circ 4'$, 18.1 volt-amperes.

(108) The primary magnetizing current of a nickel-iron-cored current transformer with bar primary, nominal ratio 100/1, operating on an external burden of 1.6 ohms non-inductive, the secondary winding resistance being 0.2 ohm, is 1.9 amp, lagging 40.6° to the secondary volts reversed, there being 100 secondary turns. With 1.0 amp flowing in the secondary calculate—

(a) The actual ratio of primary to secondary current.

(b) The phase angle between them, in minutes.

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. 101.45, 42 min.

(109) Discuss the advantages and disadvantages of using a highly permeable alloy for the construction of the cores of current transformers. Explain the meaning of the term *burden*.

A bar-type current transformer of toroidal construction requires 400 ampere-turns to magnetize it, and 300 ampere-turns to supply the iron losses, for each volt per turn induced in the secondary winding at rated frequency. Across the secondary terminals is connected an impedance of 2 ohms with a phase angle ϕ , and the resistance of the secondary winding is 0.5 ohm. The nominal ratio is 1,000/5 amperes, and it is required to minimize both ratio and phase errors. Determine the necessary values of N and ϕ , where N is the number of secondary turns.

(*Lond. Univ., Elec. Meas.*)

Ans. 194; $64^\circ 40'$.

CHAPTER XX

(110) In a test by the three-voltmeter method, the following readings were obtained: Across the mains, 180 volts; across the non-inductive resistance of 6 ohms, 88 volts; across the load, 106 volts. Calculate the self-inductance and effective resistance of the load and the power supplied to it.

Ans. Eff. res. = 5.22 Ω ; Reactance = 5.0 Ω ; Power = 1,120 W.

(111) Describe the two-wattmeter method of measuring power in a three-phase circuit.

If the readings of the wattmeter are 3 kW and 1 kW respectively, the latter reading being obtained after reversing the connections to the current coil of the wattmeter, calculate the power and the power factor.

Ans. 2 kW, 0.277.

(112) A small single-phase transformer is connected across a single-phase supply in series with a low-resistance ammeter A_1 . In parallel with the transformer and across the same terminals is connected a resistance of 100 ohms in series with another ammeter A_2 . A third ammeter A_3 is placed directly in series with the supply mains. If the readings on the three ammeters are: A_1 , 10.0 amp; A_2 , 1.0 amp; A_3 , 10.5 amp, find (a) the watts input into the transformer; (b) the power factor of the load due to the transformer.

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. 462.5 W; 0.462.

(113) The power flowing in a three-phase, three-wire, balanced-load system is measured by the two-wattmeter method. The reading on wattmeter A is 5,000 watts, and on wattmeter B is - 1,000 watts.

(a) What is the power factor of the system?

(b) If the voltage of the circuit is 440, what is the value of capacitance which must be introduced into each phase to cause the whole of the power measured to appear on wattmeter A ?

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. 0.359; 5.43 ohms.

(114) A dynamometer-pattern wattmeter has a field system which may be considered as long compared with the diameter of the moving coil. The flux density B in the field coils is 0.01 Wb/m². The mean diameter of the moving coil is 3 cm, and it is wound with 500 turns of copper wire.

If the current through the moving coil is 0.05 amp and the wattmeter is measuring the power flowing in a circuit having a power factor of 0.7, estimate the torque, if the axes of the field and moving coils are at (a) 45°, and (b) 90°.

(*A.M.I.E.E., Meters and Meas. Insts.*)

Ans. 0.89 g-cm (8.74×10^{-8} newton-metre); 1.26 g-cm (1.2×10^{-8} newton-metre)

CHAPTER XXI

(115) Show that the eddy-current torque on a metallic disc rotating between the poles of a permanent magnet is directly proportional to the angular velocity of the disc. How would the torque be expected to vary with the position of the magnet poles relative to the axis of the disc? What use is made of this device in the construction of energy meters, and what part does it play in the operating mechanism? (*Lond. Univ., Elec. Meas.*)

(116) In a simple bipolar form of a.c. energy meter, the distance between the pole centres is 1.5 cm and the effective radius of action is 2.5 cm. The fluxes produced by the series and shunt magnets are 3.5×10^{-8} and 2.75×10^{-8}

weber (r.m.s.) respectively, their phase displacement being 82° . The aluminium driving disc is 0.06 cm thick and its resistivity may be taken as 3 microhm-cm.

Neglecting the edge effect of the disc, calculate its speed if the brake magnet exerts a braking torque of 7.5×10^{-7} newton-metre when the speed is 1 revolution per minute. Frequency = 50 c/s.

Ans. 40.4 r.p.m.

(117) A large consumer has a kVA demand and a kVAh tariff, measured (by mutual agreement) by "sine" and "cosine" watt-hour type meters, each equipped with a Merz demand-indicator. The tariff is 10s. per month per kVA + $\frac{1}{2}$ d. per kVAh. Render the consumer his bill for one month of 30 days, based on the following readings: "Sine" meter advance 90,000 reactive-kVAh, demand indicator 150 reactive-kVA. "Cosine" meter advance 120,000 kWh, demand indicator 200 kW.

What are his average monthly power factor and load factor, and his total cost per unit? (A.M.I.E.E., Meters and Meas. Insts.)

Ans. 0.719d. per unit. Average load factor = Average power factor = 0.8.

CHAPTER XXII

(118) Describe a direct-reading frequency meter for measuring a frequency of the order of either (a) 50 cycles per second or (b) 500 cycles per second. Suggest a suitable method for calibrating the instrument.

(Lond. Univ., Elec. Meas.)

INDEX

- ABRAHAM-VILLARD** voltmeter, 480
Absolute—
 instruments, 634
 measurements, 71
 units, 52, 70
Absorption in dielectrics, 166, 317
A.C.—
 bridge methods, 211
 errors in, 244
 potentiometers, 359
 applications of, 368
 method of iron-loss testing, 430
 stabilizer, 369
Air—
 density factor, 472
 friction damping, 641
Ammeter—
 calibration of, 356, 368
 errors in, 657
 shunts, 710
 types of, 656
Ampere, 57
 definition of, 25
 international, 70
 legal, 71
Ampere-hour meters, 813
Ampère's theorem, 25
Amplifier-detectors, 269
Anderson bridge, 215
Anemometer, hot-wire, 310
Anode-bend voltmeter, 699
Arnold method of current transformer testing, 749
Aron clock meter, 825
Attracted-disc electrometer, 686
Attraction—
 between charged parallel surfaces, 15
 between magnetized surfaces, 24
 type moving-iron instruments, 658
Auto-repeater, 905
Ayrton universal shunt, 331
Ayrton-Perry inductometer, 258

BALANCING in instruments, 640
Ballistic galvanometer, 374
 calibration of, 380
 flux measurement with, 383
 method of capacitance measurement, 232
 method of mutual inductance measurement, 226

Bar-and-yoke methods, 401
Barlow method of measuring three-phase power, 776
Betteridge apparatus for magnet testing, 416
B-H curve, determination of, 394
Biffi method of current transformer testing, 746
Bifilar winding, 79
Biot-Savart law, 28
Bismuth spiral, 389
Blavier test, 510
Bridge measurements, source of, error in, 244
Bridge Megger, 323
Brightness, 436
Brooks and Weaver inductometer, 259
Bunsen photometer head, 442
Burrows double-bar-and-yoke permeameter, 406
Butterworth bridge, 218
Butterworth-Tinsley mutual inductometer, 261

c, determination of, 67
Cable—
 graded, 160
 multicore, capacitance of, 152
 tests with high-voltage d.c., 460, 483
 testing, 503
Cables, fault localization in, 510
Caesium resonator, 863
Cambridge reflecting wattmeter, 787
Campbell—
 bridge for iron-loss measurements, 427
 constant-inductance rheostat, 256
 frequency bridge, 867
 -Larsen a.c. potentiometer, 367
 method—
 of mutual inductance measurement, 227
 of self-inductance measurement, 239
 mutual inductometer, 260
 standards of mutual inductance, 90
 vibration galvanometer, 275
Candela, 436
Capacitance, 11
 between conducting plates, 139

- Capacitance (Contd.)—**
 between two long parallel cylinders, 141
 between two spheres, 138
 definition of, 13
 distributed, 154
 earth, 135
 geometric, 166
 measurement of, 231
 of cables, 152, 154
 of conductors parallel to earth, 147
 of systems of conductors, 136
 practical unit of, 58
 standards of, 95
Capacitance-divider method of testing voltage transformers, 755
Capacitor—
 air decade, 265
 bushing, 162
 multipliers, 715
 potential divider, 473
 square-law, 264
 variable, 262
Capacitors—
 for high voltages, 96
 in series and parallel, 151
 standard, 95
Carey-Foster slide-wire bridge, 304
Cascade connection of transformers, 465
Cathode-follower, 902
Cathode-ray oscillograph, 175, 596
 dielectric loss measurement with, 175
Celsius temperature scale, 524
C.G.S. units, 56
Chattock magnetic potentiometer, 388
Circular coil—
 magnetic field of, 31
 self-inductance of, 194
Circular turn, inductance of, 187
Clock meters, 825
Clothier and Medina method of testing voltage transformers, 756
Coaxial—
 circles, forces between, 33
 coils, mutual inductance between, 190
 cylinders, capacitance between, 146
Coercive force, 40
Commutator meters, 817
Complex wave-forms, 564
 r.m.s. value of, 586
 power with, 587
Concentric—
 circles, mutual inductance between, 187
Concentric (Contd.)—
 coils, mutual inductance between, 192
 spheres, capacitance between, 137
Constant-inductance rheostat, 256
Constant of inertia of vibration galvanometer, 275
Constant-resistance deflectional potentiometer, 349
Control—
 constant of vibration galvanometer, 276
 gear for h.v. testing, 469
 of instruments—
 gravity, 638
 spring, 636
Corona effect, 469
Coulomb, 58
Coulomb's—
 law, 1, 16
 theorem, 9
Counting-rate meter, 906
Coupling, coefficient of, 182
Coursey factor, 195
Creep of meters, 823
Crompton potentiometer, 343
Curie balance, 415
Current—
 absolute measurement of, 74
 absolute unit of, 25
 balance—
 Kelvin, 85
 Rayleigh, 77
 E.M.C.G.S. unit of, 57
 measurement of by potentiometer, 356
 transformers, 717
 characteristics of, 727
 demagnetization of, 734
 design of, 721
 errors introduced by, 720
 reduction of errors in, 731
 testing of, 743
 use of, 733
 wave-forms, 581
Current-doubling effect, 625
Cylinders—
 capacitance between, 141
 electrostatic field between, 143
Cylindrical conductors, eddy currents in, 546

DAMPED oscillations, 490
Damping—
 eddy-current, 558
 in D'Arsonval galvanometer, 337
 in instruments, 635, 641
D'Arsonval galvanometer, 333

- D'Arsonval galvanometer (*Contd.*)—
 theory of, 335
 measurement of constants, 339
- Delon mechanical rectifier, 483
- Demagnetization—
 curve, 45
 of current transformers, 734
 of magnetic specimens, 399
- Demagnetizing factors, 400
- De Sauty bridge, 233
- Detectors for a.c. bridges, 268
- Dial tests for meters, 835
- Dielectric—
 absorption, 166, 317
 breakdown, nature of, 501
 loss and power factor, 164
 measurement of, 168, 502
 strength, 159
- Dielectrics, 159
 properties of, 165
 in series, 163
- Diesselhorst potentiometer, 351
- Differential cathode-follower, 905
- Digital display, 916
- Dimensional equations, 66
- Dimensions, 53
- Diode—
 valve, 885
 voltmeter, 700
- Displacement constant of vibration galvanometer, 275
- Drysdale—
 phase shifter, 360
 plug permeameter, 410
 standard wattmeter, 801
 -Tinsley a.c. potentiometer, 360
- Ducter ohmmeter, 325
- Duddell—
 oscillograph, 590
 theory of, 592
 square-law capacitor, 264
 vibration galvanometer, 272
- Dynamometer—
 m.c. instruments, 674
 power-factor meter, 872
 wattmeter, 779, 800
- Dynatron oscillator, 890
- EARTH—
 capacitances in a.c. bridges, 246
 connections, resistance of, 327
 overlap test, 510
- Ebonite, testing of, 502
- Eddy-current—
 damping, 558, 643
 errors in a.c. bridges, 248
 loss, 417
- Eddy currents—
 effect of, 545
 in armature conductors, 556
 in cylindrical conductors, 546
 in iron core, 550
 in iron plates, 205
 in thin sheets, 548
 nature of, 545
- Electric field, 2
- Electricity Supply (Meters) Act (1936), 357, 832
- Electrodynamometers, 75
- Electrolytes, resistance of, 328
- Electrolytic meters, 808
- Electromagnetic oscillograph, 589
- Electromagnetism, 25
- Electrometer—
 attracted-disc, 686
 Kelvin absolute, 686
 Lindemann, 501
 quadrant, 682
- Electronic—
 counters, 914, 916
 high-resistance test set, 320
 repeater, 829
- Electrostatic—
 instruments, 681
 oscillograph, 596
 voltmeters, theory of, 681
 commercial forms of, 687
 for h.v., 479, 689
 wattmeter, 170, 792
- Elliott transmission system, 830
- E.M.F., induction of, 36
- Energy—
 in electric circuit, 38
 meters, 807
 practical unit of, 58
 stored in electric field, 13
 stored in magnetic field, 45
- Equipotential surfaces, 11
- Equivalent sine wave, 588
- Ewing—
 double-bar method, 403
 isthmus method, 411
- FAHY simplex permeameter, 408
- Farad, 58
- Faraday's law, 36
- Fault-localizing bridges, 518
- Faults in high-voltage cables, 487
- Feebly magnetic materials, testing of, 414
- Felici's method of mutual inductance measurement, 224
- Ferraris induction instrument, 693
- Ferric induction, 21, 373

- Fery variable-focus pyrometer, 539
 Fisher loop test, 516
 Fixed-focus radiation pyrometer, 538
 Flat coils, self-inductance of, 197
 Fleming and Clinton commutator method, 231
 Flicker photometers, 445
 Fluid friction damping, 642
 Flux—
 density, magnetic, 17
 distribution in thick iron plates, 552
 eddy-current effect on, 550
 electric, 3
 electric, tubes of, 3
 Fluxmeter, 384
 theory of, 385
 shunted, 386
 Force—
 between charged parallel surfaces, 15
 between magnetized surfaces, 24
 between parallel conductors, 30
 due to current in long straight conductor, 28
 Form-factor meter, 706
 Four-arm bridge network, 211
 Fourier's theorem, 564
 Frequency—
 bridges, 867
 errors, compensation for, 696
 in a.c. bridges, 248
 in m.i. instruments, 664
 measurement, 862
 meters, 868, 869
 standards, 862
 Friction errors in instruments, 657
 Frost-point hygrometer, 901
- GALL-TINSLEY a.c. potentiometer, 362, 430
 Galvanometer—
 ballistic, 374
 constants, measurement of, 339
 damping constant, 275
 D'Arsonval, 333
 displacement constant, 275
 inertia constant, 275
 tangent, 75
 vibration, 269
 Gas thermometers, 523
 Gauss, 58
 Gauss's theorem, 8
 Geometric capacitance, 166
 Geometrical mean distance, 188
 Giebe air capacitor, 100
 Gilbert, 58
 Giorgi (M.K.S.) system, 59
- Glazebrook and Muirhead standard air capacitor, 99
 Glynn electronic stabilizer, 836
 Grassot fluxmeter, 384
 as a quantity meter, 819
 Gravity control of instruments, 638
 Ground faults in cables, 510
 Grover series-inductance capacitance bridge, 235
 Guard rings, 157
 Guild flicker photometer, 446
 Gumlich's method of magnetic testing, 413
- HALL effect devices, 391
 Harmonic—
 analyser, 577
 analysis, 567
 Harmonics—
 even, 566
 in a.c. wave-forms, 563
 Hartshorn method of self-inductance measurement, 240
 Hay bridge, 214
 for superposed d.c. and a.c. measurements, 219
 Heaviside bridge, 118, 220
 Heaviside-Campbell bridge, 221
 Helmholtz tangent galvanometer, 77
 Henry, 58
 Heterostatic connection, 682
 Heydweiller's modification of Carey-Foster bridge, 229
 High-frequency high-voltage tests, 462
 High resistance, measurement of, 313, 320
 High voltage—
 control gear, 469
 d.c. tests, 460, 484
 high-frequency tests, 462, 489
 low-frequency tests, 460
 measurements, 471
 surge tests, 462, 494
 transformer, 464
 voltmeters, 479
 Ho and Koto oscillograph, 596
 Hobson's method of current transformer compensation, 731
 Holophane Lumeter, 452
 Hot-wire anemometer, 310
 Humidity meter, 312
 Hysteresis—
 coefficient, 43
 error in m.i. instruments, 664
 loop, 39
 determination of, 396

- Hysteresis (*Contd.*)—
 loss, 41, 399
 in small specimens, 431
 magnetic, 38
- IDIOSTATIC connection, 682
- Illiović permeameter, 404
- Illumination, 435
 definitions, 435
 laws of, 437
 photometers, 451
- Images, method of, 147, 186
- Impulse—
 ratio, 497
 tests, 462, 494
- Incremental permeability, 40
- Inductance—
 mutual, 181
 standards of, 89
 unit of, 182
 practical unit of, 58
 self-, 180
 in series, 182
 measurement of, 208
 of a wire parallel to earth, 186
 of parallel cylinders, 183
 standards of, 88, 93
 with superposed d.c. and a.c., 219
- Induction—
 ferric, 21
 instruments, 692
 method of fault localization, 521
 of e.m.f., 36
 regulator voltage control, 468
 watt-hour meters, 820
 wattmeters, 789
- Inductively-coupled ratio bridges, 242
- Inductor—
 iron-cored, 200
 variable, 257
- Instruments—
 classification of, 634
 indicating, 635
 integrating, 651
 recording, 647
 rectifier, 703
- Instrument transformers, 716
 testing of, 743
 use of, with wattmeters, 768
- Insulating—
 materials, testing of, 501
 oils, testing of, 503
- Insulation—
 resistance, 314
 measurement of, with power on, 326
 testing sets, 321
- Insulators, testing of, 498
- Integrating—
 instruments, 651
 sphere, 449
 theory of, 450
- Internal flux in conductor, 184
- International—
 conference on electrical units, 70
 temperature scale, 524
 units, definitions of, 70
- Ionic-wind voltmeter, 481
- Iron—
 loss, measurement of, 417, 424
 by a.c. potentiometer, 430
 with flux wave-form control, 426
 powders, measurements on, 428
- j*, 106
- Joule, 58
- KELVIN—
 absolute electrometer, 686
 bridge ohmmeter, 296
 current balance, 85
 double bridge, 290
 electrostatic voltmeter, 688
 temperature scale, 524
 -Varley slide, 332
- Kilovolt-amperes, measurement of, 849
- Kipping time-base, 575
- Kohlrausch method of measuring resistance of electrolytes, 328
- Kuriyama bridge, 223
- LABORATORY standards—
 capacitance, 102
 low resistance, 81, 289
- Lambert's cosine law, 437
- Laplace—
 equation, 28
 transformations, 630
- Larmor precession, 393
- Leakage—
 errors in a.c. bridges, 248
 factor, measurement of, 387
 indicators, 691
 in potentiometers, 347
- Leeds and Northrup vibration galvanometer, 273
- Left-hand rule, 29
- Legal standards, 71
- Lenz's law, 36
- Light, 435
 meter, 455
- Lindemann electrometer, 501
- Linear speed, measurement of, 861

- Lloyd-Fisher magnetic square, 419
 Logarithmic decrement, 378
 Loop tests, 513
 Lorenz method of resistance measurement, 72
 Loss angle of capacitor, 168
 Loss-of-charge method of resistance measurement, 315
 Low resistance—
 measurement of, 286
 standards, measurement of inductance of, 240
 Lumen, 436
 Lumen-hour, 437
 Luminance, 412
 Luminous—
 flux, 435
 intensity, 435
 mean horizontal, 436, 446
 mean spherical, 436, 447
 measurement of, 441
 standards, 438
 Lummer-Brodhun photometer head, 443
- MACBETH illuminometer, 451
- Magnetic—
 balance, 390, 415
 field, 17
 field due to current in a conductor, 29
 field, measurement of by Hall effect, 39
 field strength, measurement of, 389
 flux, measurement of, 383
 hysteresis, 38
 moment, 18
 permeameters, 40
 pole, 16
 potentiometer, 388
 resonance, nuclear, 392
 shells, 25
 susceptibility, 22
 testing of rods, 399
 testing with alternating current, 417
 with intense fields, 411
- Magnetization—
 curve, 22, 38
 determination of, 394
 intensity of, 18
- Magnetizing force, 21
- Magnetometers, 371
- Magnets, permanent, 45, 645
- Manganin, 83
- Marx surge generator, 494
- Maximum-demand indicators, 841
- Maxwell, 58
 bridge for determination of c , 69
 bridge for iron-loss measurements, 425
 method for mutual inductance measurement, 226
 self-inductance bridge, 212
 Maxwell's dimensions for self-inductance standard, 93
- Measuring instruments, effects utilized in, 634
- Medium resistance, measurement of, 297
- Megger insulation tester, 323
- Megger capacitance meter, 324
- Mercury—
 motor meters, 813
 thermometers, 523
- Merz-Price demand indicator, 843
- Meter testing, 832
- Meters for special purposes, 840
- Method of reversals, 394, 397
- Mica capacitors, 102
- M.K.S. units, 1, 59
- Moisture meter, 313
- Moore heavy-current wattmeter, 781
- Motor meters, 811
 errors in, 812
- Moullin thermionic voltmeter, 700
- Moving-coil instruments, 665
 design data for, 674
 errors in, 673
 extension of range of, 670
- Moving-coil vibration galvanometer, 272
- Moving-iron instruments, 658
 design data for, 665
 errors in, 660
 power-factor meters, 876
 synchroscope, 879
 theory of, 660
- Moving-magnet vibration galvanometer, 270
- Multi-core cable, capacitance of, 152
- Multipliers, voltmeter, 712
- Mumetal, 721
- Murray loop test, 513
- Mutual inductance—
 measurement of, 224
 network containing, 117
 sign of, 116
 standards of, 88
- NAGAOKA factor, 194
- Nalder-Lipman power-factor meter, 877
- National Physical Laboratory permeameter, 409

- Negative feed-back, 894
 Neon lamp, 477, 604
 Network theorems, 127
 Nickel-iron alloys, 721
 Nit, 436
 Non-inductive windings, 255
 Non-sinusoidal wave-forms, 564
 Nuclear magnetic resonance, 392
- OERSTED**, 58
 Ohm, 57
 international, 70
 legal, 71
 Board of Trade, 80
 Ohmmeter, 322
 Kelvin bridge, 296
 Evershed's Ducter, 324
 Oil, testing of, 503
 One-wattmeter method, 775
 Open-circuit faults in cables, 519
 Optical pyrometer, 541
 Oscillation method of magnet testing, 373
 Oscillators, 249
 Wien bridge, 250
 Oscillographs, 589
 Osmosis, electric, 487
 Owen bridge, 236
- PARAFFINED** paper capacitors, 102
 Parallel—
 coils, magnetic field of, 32
 cylinders—
 capacitance between, 141
 inductance between, 183
 plates, electrostatic field between, 6
 Peak—
 factor, 473
 voltage, measurement of, 475
 Pentode valve, 890
 Permanent magnets, 645
 design of, 45
 recoil loops, 47
 stabilization, 48
 testing of, 416
 Permeability—
 incremental, 40
 magnetic, 17, 21
 of free space, 55
 Permeameters, 402
 Permittivity, 1
 of free space, 55
 relative, 164
 Petch-Elliott current transformer
 testing set, 751
 pH meters, 358
 Phantom loads, 836
- Phase—
 angle—
 capacitor, 168
 current transformer, 719
 voltage transformer, 738
 error in induction meters, 822
 shifter, 360
 -splitting circuit, 364, 366
 Photo-electric cell, 453, 457
 Photometer—
 bench, 441
 heads, 442
 Pivots, friction at, 644
 Plate capacitor, capacitance of, 139
 Platinum—
 resistance thermometers, 526
 resistance variation of, 525
 temperature, 526
 Pointers, instrument, 646
 Pole, unit magnetic, 17
 Polygonal coils, self-inductance of, 198
 Polyphase—
 circuits, symbolic treatment of, 119
 meters, testing of, 839
 watt-hour meters, 825
 wattmeters, 799
 Porcelain insulators, testing of, 498
 Post-deflectional acceleration in c.r. tubes, 601
 Potential—
 at a point, 10
 connections, 286
 difference, unit of, 10
 distribution along suspension insulator string, 499
 dividers for h.v. circuits, 467
 due to a current in a closed circuit, 26
 energy of current and magnetic flux, 27
 gradient, 160
 magnetic, 23
 Potentiometer—
 a.c., 359
 constant-resistance deflectional, 349
 construction, 346
 Diesselhorst, 351
 high-precision, 353
 method of low-resistance measurement, 289
 principle of, 342
 range-changing network for, 346
 vernier, 347
 Power—
 factor meters, 872
 factor with non-sinusoidal wave-forms, 588

- Power (*Contd.*)—
 loss in instruments, 655
 measurement without a watt-meter, 770
 practical unit of, 57
 Practical electrical units, 56
 Prepayment meters, 841
 Pressure, measurement of, 309
 Price's guard-wire method, 314
 Pyrometers, 524
- Q-FACTOR and its measurement, 911
 Q-meter, 913
 Quadrant electrometer, 682
 Quantity of electricity—
 measurement of, 374
 unit of, 1, 58
 Quick-response recorders, 648, 909
- RADIANT efficiency, 435
 Radiation—
 pyrometers, 538
 Stefan-Boltzmann law of, 539
 Rationalization, 1, 59, 61
 Rayleigh—
 and Niven's formulae for self-inductance, 187
 current balance, 77
 formulae for mutual inductance, 191
 Reactive power measurement, 804
 Reason electrolytic meter, 809
 Record—
 Circscale instruments, 661, 667
 generator for speed measurement, 855
 Recording instruments, 647
 Rectifier—
 instruments, 703
 mechanical, 483
 thermionic, 484
 Reduction factor, 437
 Relay method for capacitance measurement, 232
 Remanence, 40
 Remote indication, 829
 Repulsion-type m.i. instruments, 658
 Residual—
 errors in a.c. bridges, 248
 magnetism, 39
 Residuals of resistors, 254
 Resistance—
 absolute measurement of, 72
 boxes, 252
 effective, 557
 E.M.C.G.S. unit of, 57
 high-frequency, 203
 Resistance (*Contd.*)—
 materials, 82
 measurement of by potentiometer, 354
 potential dividers, 714
 Resistors—
 measurement of self-inductance of, 239
 by Campbell's method, 239
 by Hartshorn's method, 240
 residuals of, 254
 standard, 79
 variable, 252
 Resistivity—
 of electrolytes, 328
 surface, 319
 volume, 319
 Resonance—
 curves of vibration galvanometer, 275, 283
 frequency meter, 869
 with harmonics, 585
 Reversing ratios, 304
 Ring specimens, magnetic testing of, 394
 Rotational speed measurements, 855
 Rousseau's construction, 447
 Ryall crest voltmeter, 477
- SCHERING—
 and Schmidt galvanometer, 270
 bridge, 171
 Screening—
 electrostatic, 157
 magnetic, 244
 of bridge components, 245
 Secondary instruments, 634
 Self-demagnetization, 399
 Sensitivity—
 a.c. bridges, 268
 Kelvin double bridge, 295
 Wheatstone bridge, 301
 vibration galvanometer, 283
 Servo-mechanisms, 896
 Servo-operated pen recorders, 650
 Servo-systems using velocity feedback, 899
 Shaded-pole induction instruments, 697
 Shielded high-voltage potential divider, 755
 Shielded resistor, 245
 Shielding, electrostatic, 157
 Shunts for ammeters, 710
 Siemens-Halske h.v. voltmeter, 479
 Single-phase meters, 821
 testing of, 838
 Single strip, magnetic testing of, 424

- Skin effect, 201
 in coils, 204
 in iron plates, 205
 reduction of, 203
 Smith bridge, 528
 Solenoid—
 capacitance of, 156
 magnetic field of, 34
 Sphere-gap, 471
 Spherical conductor—
 capacitance of, 137
 field inside, 4
 Spielrein formula for self-inductance, 197
 Spring control of instruments, 636
 Stabilizer, a.c., 369
 Standard—
 cells, 87
 platinum thermometer, 527
 resistors, 79
 Standards, legal, 71
 Star-delta transformation, 129
 Star-mesh transformation, general, 131
 Stefan-Boltzmann law, 539
 Steinmetz hysteresis law, 43
 Step-by-step method of magnetic testing, 396
 Straight conductors—
 capacitance between, 148
 capacitance to earth, 147
 electrostatic field near, 5
 inductance of, 186
 magnetic field near, 29
 Strain gauge measurements, 306
 Stray-field errors in a.c. bridges, 244
 Stroboscopic methods, 857
 Sub-standard lamps, 440
 Sullivan-Griffiths—
 decade air capacitor, 265
 self-inductance standard, 94
 standard capacitors, 100
 variable inductors, 262
 Summation—
 metering, 847
 methods, 801
 Summator, 848
 Superposition theorem, 128
 Supply meters, 807
 Supports in indicating instruments, 644
 Surface—
 leakage, 314
 resistivity, 319
 Surge test, 462, 494
 Swamping resistor, 670
 Symbolic notation, 106
 Symmetrical components, 122
 Synchrosopes, 878
 TACHOMETER, 855
 Tangent galvanometer, 75
 Tapped transformer for voltage control, 468
 Telephones in a.c. bridges, 268
 Temperature—
 effect on insulation, 318
 errors, 670
 indicators and recorders, 529, 535
 Tesla coil, 491
 Testing sets, 707
 Tetrode valve, 888
 Thermal converters, 676
 meters, 676
 Thermionic valve, physics of, 882
 Thermionic voltmeters, 699
 Thermo-electric—
 e.m.f., 524, 532
 in potentiometers, 355
 junction, 532
 pyrometers, 529
 Thermo-junction, 474
 Thermometers, 523
 Thermokraftfrei potentiometer, 351
 Thermopiles, 541
 Thevenin's theorem, 129
 Three-ammeter method, 210, 771
 Three-phase power measurement, 772
 Three-voltmeter method, 209, 771
 Threshold voltage, 481
 Thyatron valve, 893
 Time—
 base for cathode-ray oscillograph, 603
 constants of resistors, 254
 of electrification, effect of, 317
 switch, 844
 Toroidal coils, self-inductance of, 198
 Torque—
 dynamometer wattmeter, 783
 electrostatic instruments, 681, 683
 induction instruments, 696, 698, 790
 permanent-magnet moving-coil instruments, 665
 moving-iron instruments, 660
 Torque/weight ratio, 640
 Torsion wattmeter, 779
 Transfer error, 680
 Transformers—
 current, 717
 voltage, 735

- Transient phenomena—
 in circuits containing a number of
 meshes, 620
 with a.c., 623
 with d.c., 611
- Transistor, 918
- Triode valve, 886
- Trivector meter, 851
- Tuned detectors, 268
- Two-rate meters, 849
- Two-wattmeter method, 773
- ULBRICHT sphere, 450
- Unipivot instruments, 667
- Units—
 absolute, 52, 70
 C.G.S., 52, 57
 international, 70
 M.K.S., 59
 practical, 56
 rationalized systems, 61
- Universal shunt, 331
- Unrationalized C.G.S. formulae, 48
- VACUO-thermo-junctions, 677
 precision measurements with, 679
- Vacuum-enclosed electrostatic volt-
 meters, 689
- Valve rectifier, 484
- Variable—
 capacitor, 262
 inductor, 257
 resistor, 252
- Varley loop test, 515
- Velocity feed-back, 897
- Vernier potentiometer, 347
- Vibration galvanometer, 269
 natural frequency of, 278
 theory of, 274
- Volt, 57
 box, 356
 international, 70
 legal, 71
- Voltage—
 measurement by potentiometer,
 356
 regulation, 465
 standardizer, 357
- Voltage-amplifier, pentode, 891
- Voltage-drop tests on cables, 512
- Voltage transformers, 735
 characteristics of, 741
 design considerations, 739
- Voltage transformers (*Contd.*)—
 errors introduced by, 739
 testing of, 752
- Voltmeter—
 calibration of, 356, 368
 errors in, 657
 multipliers, 712
 thermionic, 699
- Volume resistivity, 319
- WAGNER earthing device, 247
- Water purity, measurement of, 329
- Watt, 57
 international, 70
- Watt-hour mercury meters, 816
- Wattmeter—
 calibration by electrostatic watt-
 meter, 797
 connections, 767
 correction factor, 765, 770
 electrostatic, 170, 792
 errors, 764
 induction, 789
 measurements in single-phase
 circuits, 764
 method of iron-loss measurement,
 419
 polyphase, 799
 reflecting, 787
 theory of, 783
 testing of, by a.c. potentiometer,
 368
 types of, 779
- Wave-filter, 249
- Wave-form, 563
 current, 581
 determination of, 589
 errors in a.c. bridges, 248
- Weber, 58
- Weighing, electric, 308
- Weston—
 frequency meter, 871
 standard cell, 87
 synchroscope, 878
- Wheatstone bridge, 298
 precision measurements with, 302
 applications of, 306
- Wien bridge, 114, 237
- Wind-direction indicator, 901
- Work-function, 884
- Wright—
 electrolytic meter, 809
 maximum-demand indicator, 841