

Index

- Accuracy of short-circuit calculations, 528
- Addition, of admittances, 158, 159
of complex waves, 261
of currents, 128
of impedances, 142, 143, 158
of vectors, 68
of voltages, 68, 128
of volt-amperes, 347, 395
- Admittance, addition of, 158, 159
definition, 158
surge, 418
- Air-core transformer, 291, 314, 317
vector diagram, 295, 315, 316
- Algebra of phasors, 107
- Alternating current, amount used in United States, 45
ampere value, 85
average value, 86, 88
beginning of systems, 45
components of, 99
definition, 47, 48
effective value, 87
equation of, 51
four-phase systems, 328
generation of, 45, 46
lagging, 52, 53
sine-wave representation, 51, 91
three-phase, 331, 334
two-phase systems, 328
- Alternating volt, definition, 86
- Alternating voltage, components of, 99
definition, 47, 48
see also Alternating current
- Amplitude factor, 89
- Analysis, methods of, loop-current, 7, 274, 377
nodal, 198
node-pair, 15-22
- Analysis of non-sinusoidal waves, 225
analytical method, 228
analyzing tables, 237-240
graphical method, 233, 242
rectangular wave, 231, 232
triangular wave, 231, 232, 233
- Analytical method for determining whether two waves are of the same form, 248-250
- Angular frequency, 50
- Angular velocity, 50
- Attenuation, 136
band, 435
constant or factor of a filter section, 449
constant or factor of a long transmission line, 417
decibels of, 136, 451
frequency of infinite, 481
general, 136
method of expressing for filter, 449-453
nepers of, 136, 450, 451
see also Filters, high- and low-pass
- Auto-transformer, air-core, 317
- Average value of a wave, 86, 88
- Balanced delta load, 339
- Balanced delta system of currents, 334, 335
- Balanced systems, power in, 343, 344, 349
- Balanced wye load, 337
- Balanced wye system of currents, 333
- Band, side, 266
- Band-eliminator filter, 473, 474
- Band-pass filter, definition, 473
- Bands, pass or transmission, 435
stop or attenuation, 435
- Bases for expressing impedances, 523
- Boundary conditions, 550

- Branch, 5
 - link, 23
 - tree, 23
- Capacitance, effect of in a circuit, 62-66
 - energy stored in, 65
 - impedance due to, 63
 - phasor diagram, branch of, 94
 - tables of, for transmission lines, 430
 - transmission line, 425
 - vector diagram, branch of, 94
- Capacitive coupling, 276
- Capacitive reactance, 63
- Capacitive susceptance, 159-163
- Carrier frequency, 264, 266
- Cartesian form, of impedance, 125
 - of operator, 108, 109
- Characteristic impedance, 439
 - determination from open- and short-circuit impedances, 443
 - low-pass constant- k , π -section, 466
 - T-section, 466
 - π -section, 440
 - T-section, 440
 - variation of for constant- k sections, 467
- Circle diagram of series circuit, 155
- Circuit, capacitive only, 62-66
 - coupled capacitively, 276
 - coupled conductively, 273
 - coupled mutual inductively, 278
 - definition, 273
 - direction, 7, 46, 95, 129, 379
 - inductive only, 59, 94
 - parallel, 158
 - polyphase, 325
 - resistive, inductive, and capacitive, 75
 - resistive and capacitive, 74
 - resistive and inductive, 66
 - resistive only, 57, 93
 - series, 142
 - series-parallel, 174
 - sweep, 557
- Coefficient, of coupling, 277, 283
 - of mutual inductance, 279
 - of self-inductance, 279-280
- Coil, iron-core magnetizing current of, 224
- Complex frequency, 179, 572
- Complex notation, 107
 - Complex waves, 223
 - addition of, 261
 - components of, 225
 - definition, 225
 - subtraction of, 261
 - Conditions, boundary, 550
 - Conductance, 15, 160
 - matrix, 20, 21
 - Conductive coupling, types of, 273-276
 - Conductively coupled circuit, 273
 - Conjugates of voltage and current, 132, 133
 - Connection checks, for wattmeters, 350, 352
 - Constant- k filter, *see* Filters, constant- k type
 - Copper, comparison of requirements for transmission, 358-360
 - Coupled circuits, 273
 - design, 309
 - equations of voltage for, 282
 - impedance of, 299
 - loose, 283
 - maximum current in, 306
 - partial resonance of, 303
 - resonance of, 301-314
 - Coupling, capacitive, 276
 - coefficient of, 277, 283
 - conductive, 273, 276
 - critical, 306
 - inductive, 278
 - loose, 283
 - mutual inductance, 278
 - range of, 283
 - resistance, 276
 - Crest factor, 89
 - Critical coupling, 306
 - Current, alternating, definition, 46, 47, 48
 - average value, 86, 87, 88
 - components of, 99
 - effective value, 85, 88
 - fault, 522
 - instantaneous, 51, 78, 91, 261
 - in parallel branches, 158
 - loop, or mesh, 7, 274, 377
 - resonance, 162-168
 - rms value, 85, 88
 - in series branches, 142
 - for non-sinusoidal voltages, 256-262

- Current, in series-parallel branches, 174-176
 for series resonance, 145, 146
 source, 1, 3, 199, 200
 virtual value of, 85
- Current loci, for parallel branches, 164, 165
 for series branches, 155-158
- Currents, addition of, 128
 subtraction of, 128
- Cut-off frequency, 454, 463, 465, 481
- Cycle, 48
- Decibel, definition of, 451
- Degrees of symmetry of waves, 246
- Delta connection, balanced load, 339
 current for, 334, 335
 equivalent for wye, 206-211
 harmonics in, 365
 symmetrical components of phase currents, 502, 503
 unbalanced, current relations, 400
 solution of, 373, 381
 voltage, 334
- Delta-wye conversion, 207, 382
- Delta and wye loads combined, solution of, 376
- Deviation factor, definition of, 256
 determination of, 256
 use, 256
- Directions, circuit, 7, 46, 95, 129, 379
- Direct wave of a transmission line, 417
- Displaced a-c wave, effective value of, 562
- Distorted waves, 223
- Distributed parameters, 413
- Division of phasors or vectors, 119
- Dot-marked terminal, 286
- Double-subscript notation, 327
- Drain, high-frequency line, 435
 low-frequency line, 436
- Dual networks, 31
- Duality, 29, 32, 400
- Effective value, 85, 88
 current, 85, 86, 88
 displaced a-c wave, 562
 non-sinusoidal wave, 250
 sinusoid, 88
 voltage, 86, 88
- Electric wave filters, 435
- Energy, stored in capacitance, 65
 stored in inductance, 62
- Equivalent current source, 3, 4, 199, 200
- Equivalent delta for wye, 206, 207, 210
- Equivalent equilateral spacing for transmission lines, 428
- Equivalent plate circuit of vacuum tube, 203
- Equivalent sine waves, 255
 phase difference of, 255
- Equivalent wye, for delta conversion, 206
 formula for, 207
- Euler's equation, 110
- Even harmonics, effect of, 246-248
- Evolution of a phasor or vector, 121
- Experimental determination, of currents in polyphase loads, 400
 of voltages in polyphase loads, 400
- Exponential, complex, 179, 573-575
- Exponential operator, 110
- Factor, amplitude, 89
 crest, 89
 deviation, 256
 form, 88
 peak, 89
 power, definition, 99
 see also Power factor
 reactive, 99, 345
 transfer, 300
- Fault, defined, 522
- Fault currents, solving for, 528, 531, 539
- Faults, kind of, 522
- Filters, attenuation constant, 449-453
 band-eliminator, 473, 474
 definition, 474
 band-pass, definition, 473
 comparison of characteristics of constant- k and m -derived types, 481
 constant- k type, definition, 464
 high-pass, cut-off frequency, 468
 design equations, 468-469
 summary of characteristics, 471, 472
 limitations, 474
 low-pass, characteristic impedance, 466
 cut-off frequency, 465

- Filters, constant- k type, low-pass, design equations, 466, 467
 summary of characteristics, 471, 472
 zero-frequency value of impedance, 466
- definition, 435
 electric wave, 435
 full m -derived, 480
 attenuation and phase shift, 483
 effect of cut-off and infinite attenuation frequencies on value of m , 438
 frequencies of infinite attenuation, 481
 high-pass, 482
 low-pass, 481, 482
- fundamental equation of, 454-456
 general design procedure, 484
 half section, 475-479
 high-pass, attenuation, 461
 definition, 454
 low-pass, attenuation, 458
 definition, 454
 m -derived half sections, 475
 characteristic impedance, 477
 general equations of, 477, 478
 open-circuit impedance, 439, 443
 phase constant β , 449, 450
 phase shift, 455, 458, 461
 π -section, 440
 propagation constant, 449
 short-circuit impedance, 439, 443
 T-section, 440
 without resistance, 457
- Finite differences, method of solving equations by, 585
- Flux, in iron-core transformer, 581-585
 leakage, 279, 314
 mutual, 279, 314
- Form factor, 88
- Foster's reactance theorem, 188
- Fourier analysis, general, 225
 analytical method, 228
 analyzing tables, 237-240
 graphical method, 233-242
 rectangular wave, 231-233
 triangular wave, 228-232
- Fourier series, 225
 coefficients of, 227
- Four-phase systems, 328
- Four-terminal network, 438
- Four-wire, three-phase system, 331
- Frequency, 48, 49
 angular, 50
 carrier, 264, 265
 common for power use, 49
 complex, 179, 572
 components of modulated waves, 264, 265
 cut-off, 454, 463, 465, 468, 481
 infinite attenuation for filters, 481
 oscillatory, 570
 range of pass band for RLC circuit, 152
 resonant, for parallel branches, 160
 for series circuit, 145
- Generation of alternating current, 45, 46, 325
- Geometric mean spacing of transmission conductors, 428
- Graphical composition of symmetrical components, 493
- Graphical method, for rms value determination, 86
 for wave analysis, 233, 242
- Half-power points, 152
- Half-wave resonance, 418
- Half-wave symmetry, 246, 247
- Harmonics, caused by variation of circuit parameters, 262
 components of a complex wave, 225
 in a delta system, 365
 effect of even on a wave, 246, 248
 in a wye system, 361
- High-pass filter, *see* Filters
- Image basis of termination of filter section, 442
- Image impedance, 438
- Impedance, base, 523
 capacitive, 63
 cartesian form of, 125
 characteristic, for filters, 439
 for T- and π -sections, 440
see also Characteristic impedance
 coupled circuit, 299
 diagram for series RLC branch, variable capacitance, 149

- Impedance, variable frequency, 150
 variable inductance, 147
 function, defined, 56
 image, 438
 inductive, 60
 matching, 192
 mutual, 273, 281
 negative-sequence, 510-511, 533, 535
 negative-sequence component of, 509
 open circuit of a filter, 439, 443
 percentage of, 525
 polar form of, 124
 positive-sequence, 510, 533, 535
 positive-sequence component of, 509
 rectangular form of, *see* Impedance,
 cartesian form of
 referred to a common base, 523
 reflected, 299, 300
 resistive, 57
 resistive, inductive, and capacitive, 75
 resistive and capacitive, 75
 resistive and inductive, 69
 short-circuit, of filter, 439
 surge, 418
 transfer, 197
 transfer factor, 300
 transferred, 298
 zero-sequence, 535, 540
 of generators, 535, 540
 of transformers, 541
- Impedance, zero-sequence, of transmission lines, 542
 zero-sequence component of, 509
- Impedances, addition of, 142, 143, 158
 parallel, 158
 series, 142, 143
 series-parallel, 174
- Inductance, coefficient of mutual, 279
 coefficient of self-, 279, 280
 effect of, 60
 energy stored in, 62
 leakage, 316
 mutual, 279
 definition, 280
 phasor diagram of branch, 94
 transmission line, formula, 425
 general, 423
 transmission line table, 429
 vector diagram of branch, 94
- Inductive coupling, 278
- Inductive reactance, 60
- Inductive susceptance, 158-162
- Infinite-frequency characteristic impedance, 469
- Instantaneous currents, combination of, 78, 91, 92
- Instantaneous power, 57, 61, 63-65, 70, 71, 348
- Instantaneous value of current and voltage, 51, 52
- Involvement of a phasor, 122
- Iron-clad RL circuit, transients in, 581
- Iron-core coil, current in, 224
- j , operator, 107
- Kilovolt-amperes, 99
- Kirchhoff's laws, application of, 30, 377
- Kirchhoff's law, application to alternating current, 377
- Ladder structures, 453
- Lagging current, 53-55
- Leakage flux, 279, 314
 inductance, 316
- Line calculations, approximate methods, 410-413
 exact method, 413
- Line constants, formulas for, 425-428
 cables of, 429, 430
- Line drain, high-frequency, 435
 low-frequency, 436
- Line-to-ground short circuit, 539
- Line-to-line short circuit, 531
- Links, 23
- Logarithm of a phasor, 123
- Loop current solution, 7, 274, 377
see also Mesh, current solution
- Loose coupling, 283
- Lower side-band, 266
- Low-pass constant- k filter, *see* Filters,
 constant- κ type
- Low-pass filter, *see* Filters
- Magnetic coupling or mutual inductive coupling, 278
- Magnetic coupling between phases, 515-518
- Magnetizing current of iron-core coil, 224
- Matching of impedances, 192

- Matrix, 10, 12
 conductance, 20
 determinant of, 11, 12
 resistance, 11, 13-15
- Maximum power transfer, 192-193
- m*-derived filter section, full, 480
- m*-derived half section, 473
- Measurement, of power in balanced systems, 349
 of reactive volt-amperes, 344, 396-398
 of three-phase power by three wattmeters, 387, 388
 of three-phase power by two wattmeters, 349, 389
- Mesh, 23
 connection, general, 334, 335
 current solution, 274
 four-phase, 330
n-phase, 336
 three-phase, *see* Delta connection
- Mho, 15, 159
- Modulated waves, composition of, 264, 265
- Modulation, definition of percentage, 265
- Multiplication of phasors, 116
- Mutual flux, 279, 314
- Mutual inductance or induction, 279
 between parallel branches, 289
 between series branches, 286
 coefficient of, 279
 definition, 279
 impedance, 273, 281
 reactance due to, 281
 sign of, 284
- Mutual induction voltage, 281
 direction of, 284
- Mutual inductive coupling, 278, 279
- Napier, definition, 451
- Negative-sequence components, 490, 492
 evaluation, 495
 impedance component, 510
- Negative-sequence impedances of rotating machines, 533-536
- Neper, definition, 136, 450, 451
- Network, image impedance, 438
 smoothing, 436, 438
 theorems, 194, 196, 197, 205
 topology, 22
 variables, 6
- Networks, 194
 dual, 31
 π , 211
 T, 211
 theorems, 194, 196, 197, 205
- Nodal method of circuit solution, 15-22, 198
- Node, 7, 199
- Node-pair voltages, 15
- Non-linear parameters, step-by-step solutions, 585-589
- Non-sinusoidal waves, 223
 circuit analysis for, 225, 256, 258
 effective value of, 250
 expressing, 225
 parallel circuit analysis for, 258
 power calculations for, 252
 power factor for, 254
 series circuit analysis for, 256
 shifting the phase of, 249
 volt-amperes of, 254
- Norton's theorem, 205
- Notation, double-subscript, 327
- n*-phase mesh, 336
- n*-phase star, 336
- Ohmic method of short-circuit calculations, 523
- Open-circuit impedance of a filter, 439, 443
- Open-line check, 352
- Operator, cartesian form, 108, 109
 exponential, 110
j, 108
 polar form, 111
 rectangular form, 110
- Oscillatory term of *RLC* circuit, 568, 569, 580
 frequency of, 570
- Parallel, impedances in, 158
- Parallel branch analysis, 158
 for non-sinusoidal waves, 258
- Parallel branch current loci, 164-166
- Parallel branches, resonance in, 162
- Parallel branch resonance for all frequencies, 170
- Parallel resonance, 162-168
 by varying *C*, 165
 by varying *f*, 166

- Parallel resonance, by varying L , 163
 by varying R_c , 167
 by varying R_L , 167
- Parameters, distributed, 413
 effect of variation on wave form, 262
 non-linear, step-by-step solution, 585-589
 transmission line, 423
- Partial resonance of coupled circuits, 303
- Pass band, boundary of, for filters, 458-465, 473, 481
 definition, for filters, 435
 for series RLC circuit, 151
 width of, for series RLC circuit, 152
- Peak factor, 89
- Percentage method of expressing parameters, 525
- Percentage of modulation, 265
- Percentage reactance, 526
- Percentage resistance, 526
- Period, definition, 48
- Per unit method of expressing parameters, 528
- Phase, 52
 angle, 52
 constant, of a filter, 449
 of a long line, 418, 421
 of current and voltage, 57, 60, 63, 67, 69, 75
 difference, 53
 for equivalent sine waves, 255
 magnetic coupling between phases, 515-518
 n -phase mesh, 336
 n -phase star, 336
 sequence, 326, 327, 339
 effects, 383
 impedances, 509, 510, 533, 540
 methods of checking, 383, 384
 shift, general, 137
 of high-pass filter section, 461
 of low-pass filter section, 458
 shifting of a non-sinusoidal wave, 249
- Phasor, 90
- Phasors, addition of, 112
 algebra of, 107
 cartesian form of notation for, 108
 division of, 119
 evolution of, 121
 involution of, 122
- Phasors, logarithm of, 123
 multiplication of, 116
 raising to powers, 121
 rectangular form of notation for, 108
 representing sine waves, 90
 root of, 122
 subtraction of, 114
- π -network, 211
- π -section filter, 440
 attenuation of, 455
 characteristic impedance, 440, 443
 phase shift, 455
- Polar form, of impedance, 123
 of operator, 111
- Polarity marks, 286
- Poles, 182, 572
- Polyphase, generation of voltages, 325
 see also Mesh, Star connection, Delta connection, Wye, n -phase mesh
- Polyphase power, balanced systems, 343
 comparison with single-phase power, 348
 unbalanced systems, 387-390
 see also Power
- Polyphase unbalanced, general, 373, 377
- Positive directions of voltages and currents, 95, 128, 284
- Positive-phase sequence system, 489, 491
 evaluation of, 494, 533
 impedance of rotating machines, 534, 535
 impedance of static elements, 509
- Power, half-power points, 152
 instantaneous, 57, 61, 63-65, 70, 71, 348
 maximum from circle diagram, 157
 maximum transfer in a series circuit, 192
 measurement, of balanced polyphase, 349
 in an n -wire system, 357, 392
 by three-wattmeter method, 387
 by two-wattmeter method, 349, 387-390
- in a purely capacitive branch, 64
 in a purely inductive branch, 61
 in a purely resistive branch, 58
 reactive, in general, 96
 real; in general, 96
 in a resistive and inductive branch, 70

- Power, in an *RLC* branch, 76
 system short-circuit calculations, 522
 three-phase, 343, 387-390
 of a phasor, 121
- Power calculation, of balanced poly-phase, 343
 of balanced three-phase, 343
 from complex forms, 131
 from conjugate of V and I , 133
 for non-sinusoidal waves, 252
 of single and three-phase, 348
- Power factor, balanced three-phase, 345
 definition, 99, 345
 for non-sinusoidal waves, 254
 of series branch, 143
 in unbalanced polyphase systems, 394
- Power formula, for balanced three-phase, 343, 345
 for single-phase, 96
- Propagation, velocity of, 419
 of a wave, 417
- Propagation constant, of a filter, 449
 of a long line, 417
- Q , of a coil, 153
 of a parallel circuit, 171
 of a series circuit, 153
- Quarter-phase, *see* Four-phase systems
- Quarter-wave resonance of a long line, 418
- Quarter-wave symmetry, 247
- Range of coupling, 283
- RC* branch, transients, 553
- Reactance, capacitive, 63
 inductive, 60
 mutual, 281
 percentage, 526
 per unit, 525, 528
- Reactive factor, 100, 345
- Reactive power, *see* Reactive volt-amperes
- Reactive volt-amperes, 71, 96, 344
 balanced three-phase, 344
 calculated from complex expressions, 131
 determination from conjugates of V and I , 133
 formula, for balanced three-phase, 344, 345
- Reactive volt-amperes, formula, for single-phase, 97
 measurement, of balanced three-phase, 353
 in unbalanced four-wire, three-phase, 392
 sign of, 76, 97
- Reciprocity theorem, 196
- Rectangular form, of impedance, 125
 of operator, 109, 110
- Rectangular wave, 231, 233
- Rectifier, constants for smoothing network of, 437, 438
 smoothing network for, 436, 438
- Reflected impedance, 299, 300
- Reflected wave, 417, 418
- Reflections, terminal of a line, 419
- Resistance, effect of, 57
 impedance due to, 57
 percentage of, defined, 526
 in series, with capacitance, 75
 with inductance, 69
 with inductance and capacitance, 75
 vector diagram of branch, 93
- Resistance coupling, 276
- Resonance, in coupled circuits, 301-314
 of a long transmission line, half-wave, 418
 quarter-wave, 418
 three-quarter-wave, 418
 in parallel circuits, 162
see also Parallel resonance
 series circuits, 144
see also Series resonance
- RL* branch transients and steady current
 in, for alternating current, 558
 for direct current, 551
- RLC* branch, selective properties, *see* Selective *RLC* circuit
 vector diagram, 95
- RLC* series branch, equation of current, 579
 oscillatory term of, 580
 transients in, 566, 571, 576
 for $R^2/4L^2 > 1/LC$, 568, 571, 579
 for $R^2/4L^2 < 1/LC$, 568, 571, 580
- RL* iron-clad circuit, transients in, 581-585
- rms value, 85, 88
 of a displaced sinusoidal wave, 562

- rms value, graphical determination of, 86
 of a sinusoidal wave, 88
 Root of a phasor, 122
- Sawtooth wave form, 555
- Selective properties of circuit elements, 435
 high-frequency line drain, 435
 low-frequency line drain, 436
- Selective *RLC* circuit, 151
 pass band, definition, 151
 width of, 152
- Selectivity of *RLC* series branch, 152, 153
- Self-inductance, 279
 voltage of, 282
- Sequence, phase, 326, 327, 339
 checking, 383
 effects of, 383
 negative-phase sequence system, 490, 492, 495
 impedance, 509, 533-536
 positive-phase sequence system, 489, 491, 494
 impedance, 509, 534, 535
 rule, 512, 513
 zero-phase sequence system, 490, 492, 495
 impedance, 509, 535, 540, 541, 542
- Series, impedances in, 142
 resonance, 144
- Series branch, 142
 circle diagram, 155
 efficiency of for transmission, 157
- Series circuit, 142
 analysis for non-sinusoidal waves, 236
 circle diagram of, 155
 current loci, 155, 156
 maximum power transfer of, 192
- Series-parallel branches, 174
- Series-parallel tuning, 176
- Series resonance, 144
 frequency for, 145
 by varying capacitance, 148
 by varying frequency, 149
 by varying inductance, 146
 voltage drops, 145
- Shifting the reference point of a non-sinusoidal wave, 249
- Short circuit, accuracy of calculations, 528
 calculation, by ohmic method, 523
 by percentage method, 525
 by per unit method, 528
 in power systems, 522
 impedance of a filter, 443
 definition, 439, 443
 line-to-ground, 539
 calculation of, 539, 544
 line-to-line, 531
 calculation of, 536
- Side bands, 266
- Sign of readings of wattmeters, 350-353
- Sine wave, representation of alternating current, 50
- Sine waves, equivalent, 255
- Sinusoidal wave, average value of, 88
 crest factor of, 89
 effective value, 85, 88
 form factor, 88
 vector representation of, 90
- Smoothing network, 436, 438
 constants for, 437
- Sources, current, 2, 3
 ideal voltage, 4
 voltage, 1, 3
- S-plane, 181, 184, 187
- Star connection, general, 336
 four-phase, 329
n-phase, 336
 three-phase, 331, 332
- Steady-state term, 551, 553, 560, 561, 565, 580
- Step-by-step method solution for non-linear parameters, 585-589
- Stop band, 435
- Subtraction, of currents, 128
 of phasors, 114
- Superposition, principle, 5, 20
 theorem, 194
- Surge admittance, 418
- Surge impedance, 418
- Susceptance, 159-162
- Sweep circuit, 557
- Symbolic notation, *see* Phasors, algebra of
- Symmetrical components, 489
 copper losses from, 508
 delta-wye voltage transformations, 500
 graphical composition of, 493

- Symmetrical components, line-to-ground
 current representation, 504, 505
 negative-sequence system, 490, 492
 evaluation, 495, 533
 impedance, for rotating machines,
 535
 for static elements, 509
 of phase currents in delta-connected
 loads, 502
 positive-sequence system, 489, 491
 evaluation, 494, 533
 impedance, for rotating machines,
 535
 for static elements, 509
 power from, 506-508
 solution for fault currents, 522-546
 unbalanced current representation,
 502-506
 unbalanced line voltage representation,
 497, 500-501
 use of, 489
 zero-sequence system, 490, 492, 495
 evaluation, 494-496, 533, 539
 impedance, for rotating machines,
 533-535, 540-541
 zero-sequence system, impedance, for
 static elements, 509
- Symmetry, of complex waves, 246
 degrees of, 246
 half-wave, 246
 non-sine waves, 246
 positive and negative loops, 246
 quarter-wave, 247
 of wave about its 90° ordinate, 247
- Systems, four-phase, 328
 three-phase, 331-336
 two-phase, 328
see also Alternating current
- Tables, of capacitance for transmission
 lines, 430
 of inductance for transmission lines,
 429
- Terminal reflections, 419
- Termination of filter section on image
 basis, 442
- Thévenin's theorem, 197
- Three-origin vector diagram, 341
- Three-phase, four-wire system, 331
- Three-phase, three-wire system, 334
- Three-phase power measurement, 387-
 390
- Three-quarter-wave resonance of a long
 line, 418
- Three-wire, two-phase system, 331
- Time constant, of RC branch, 555
 of RL branch, 552
- T-network, 211
- Topological warping, 23
- Topology, 22
- Transfer factor, 300
- Transfer impedance, 135, 197
- Transferred impedance, 298
- Transformer, air-core, 291-298, 314-
 317
 vector diagram of, 315, 316
 air-core auto-, 317
- Transient, application of, 549
 defined, 549
 sawtooth wave, 555-558
- Transients, of RC branch, 553
 of RL branch, 549, 581
 of RLC series circuit, 566-581, 582
 oscillatory frequency of, 570, 572,
 580
 $R^2/4L^2 > 1/LC$, 568, 571, 579
 $R^2/4L^2 < 1/LC$, 568, 571, 580
 of RL iron-clad circuit, 581-585
- Transmission, 184
- Transmission band, 435
- Transmission line, general, 409
 approximate solution, by Steinmetz
 method, 412
 exact solution, 413
 geometric mean spacing of conductor,
 428
 by π -line, 411
 representation of, 409
 by T-line, 410
- Transmission line parameters, 423
 capacitance, formula, 428
 table, 430
 derivation of formulas, 423, 425
 inductance, formula, 425
 table, 429
- Transmission of power, comparison of
 copper requirements, 358-360
- Tree, topological, 23
- Triangular waves, analysis of, 231-233
 equation of, 229, 232, 233

- T-section, filter, 440
 attenuation of, 455, 458, 461
 characteristic impedance of, 439-441, 443
 phase shift, 449, 455, 458, 461
 series arm, 456
 shunt arm, 456
- Tuning, series-parallel, 176
- Two-phase systems, 328
- Two-wattmeter method of measuring
 3-phase power, 349, 387-390
- Unbalanced currents, representation by
 symmetrical components, 502-506
- Unbalanced polyphase circuits, general,
 373, 377
 delta, solution of, 382
 power factor of, 394-396
 solution by Kirchhoff's laws, 377
 wye-wye with neutral solution, 381
 wye-wye without neutral solution,
 377, 379
- Unbalanced voltage, representation by
 symmetrical components, 497-502
- Upper side band, 266
- Var, 72, 98
- Varmeter, 72
see also Reactive volt-amperes, meter
- Vector, 90
- Vector algebra, *see* Phasors, algebra of
- Vector diagrams or phasor diagrams,
 general, 94, 97
 C-branch, 94
 L-branch, 94
 R-branch, 93
 RC-branch, 95
 RL-branch, 94
 RLC-branch, 95
 three-origin, 341
- Vector volt-amperes, 394, 395
- Velocity, angular, 50
 of wave propagation, 419
- Virtual value of current or voltage, 85
- Volt, alternating defined, 86
- Voltage, alternating, components of,
 99
 definition, 45, 46
- Voltage, drop, 95
 drops, across series-parallel branches
 174
 at series resonance, 145
 equations of coupled circuits, 282
 instantaneous, 51
 mutual, direction of, 284
 mutual induction, 279
 node-pair, 7, 15
 resonance, 144
 rise, 95
 self-induced, 282
 series branch for non-sinusoidal waves,
 256
 source, 1, 3
- Voltages, addition of, 102, 103, 127
 delta, 334
 generation of polyphase, 325
 vector addition of, 127, 128
 vector combination of, 102, 103, 127
 vector subtraction of, 102, 103, 127
 wye, 332
- Volt-amperes, 99, 344
 addition of, 394, 395
 balanced three-phase, 344
 non-sinusoidal waves, for, 254
 reactive, 71, 96, 132, 133
 in three-phase, 344, 392
 vector, 394, 395
- Warping, topological, 23
- Wattmeters, checking signs of, 352, 353
- Watt-ratio curve, 352
- Wave, sawtooth, 555
- Wave analysis, 225
 analytical method, 228
 graphical method, 233, 242
- Wave form, 47, 246, 248, 251
 of current in an iron-core coil, 224
- Wave-length constant, of a filter, *see*
 Phase constant, of a filter
 of a long line, 418, 421
- Wave propagation, velocity of, 419
- Waves, addition of complex, 261
 attenuation of, 417
 complex or non-sinusoidal, 223, 225
 composite, 223, 225
 direct, 417, 418
 modulated, 263
 propagation of, 417, 419

- Waves, rectangular, 231, 233
reflecte.l, 417, 418
of same shape or form analytical
method of determining, 248
sawtooth, 555
subtraction of, 91, 92, 261
triangular, 231, 233
- Wave shape, 47, 50, 246-251
effect of shifting an harmonic on, 248,
250, 251
- Wave trap, 169
- Weber-turns, 281
- Wye, general, 332, 336
and delta loads combined, solution
of, 376
balanced load, 337
connection, voltages and currents in,
332, 333
magnetic coupling between phases
of, 515-518
- Wye-delta, conversion, 206-210, 374, 375
- Wye-delta, unbalanced, solution of,
382
- Wye system, currents in, 333
harmonics in, 361
- Wye-wye system, unbalanced, with
neutral, 381
without neutral, 377-380
- Y, see Wye
- Zeros, 182, 572
- Zero-frequency characteristic impedance,
466
- Zero-sequence component of impedance,
509
- Zero-sequence impedance, of rotating
machines, 535, 540
of transformers, 541
of transmission lines, 542
- Zero-sequence system, 490, 492, 495
evaluation of, 495, 496